
 



# AHB-Lite System Integration

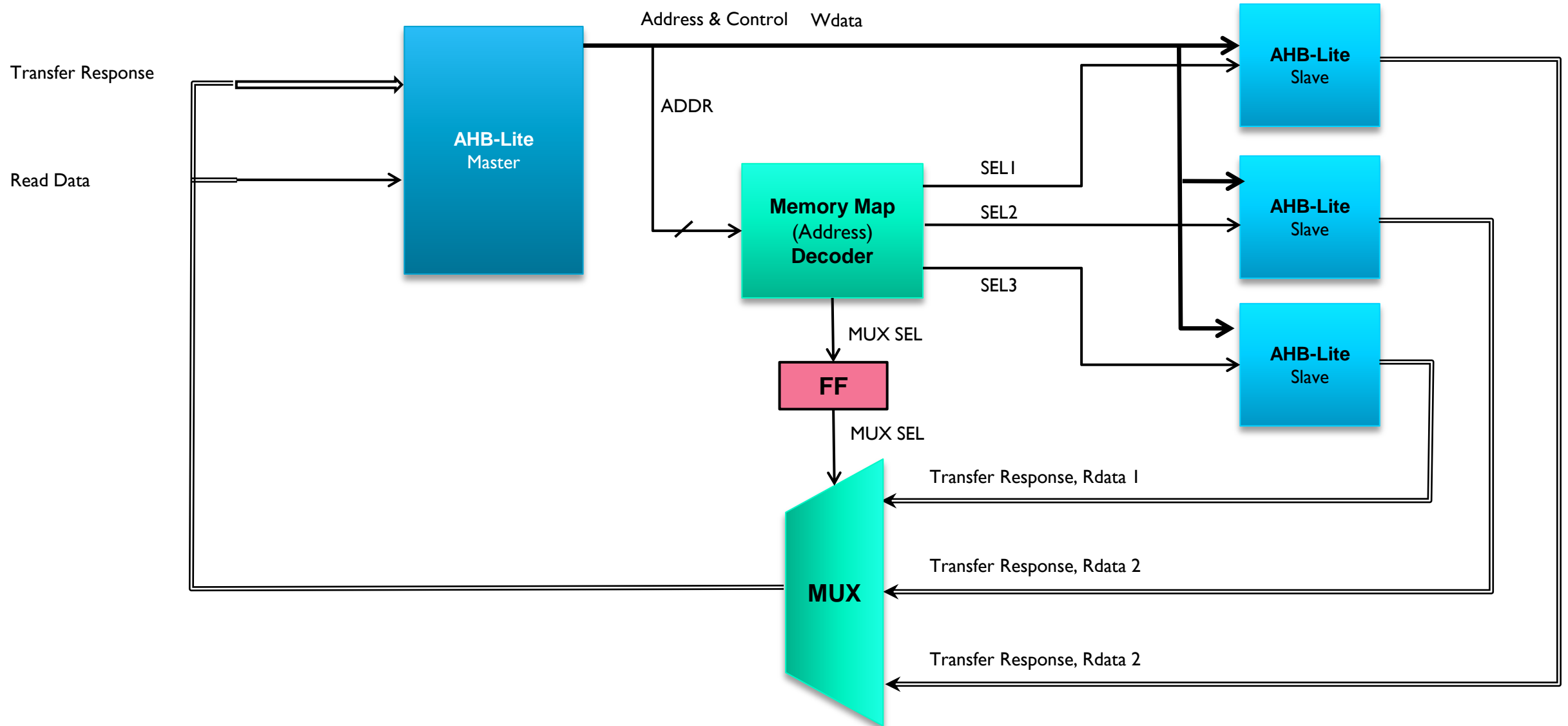

# AHB-Lite System (Recap)



# Basic SoC

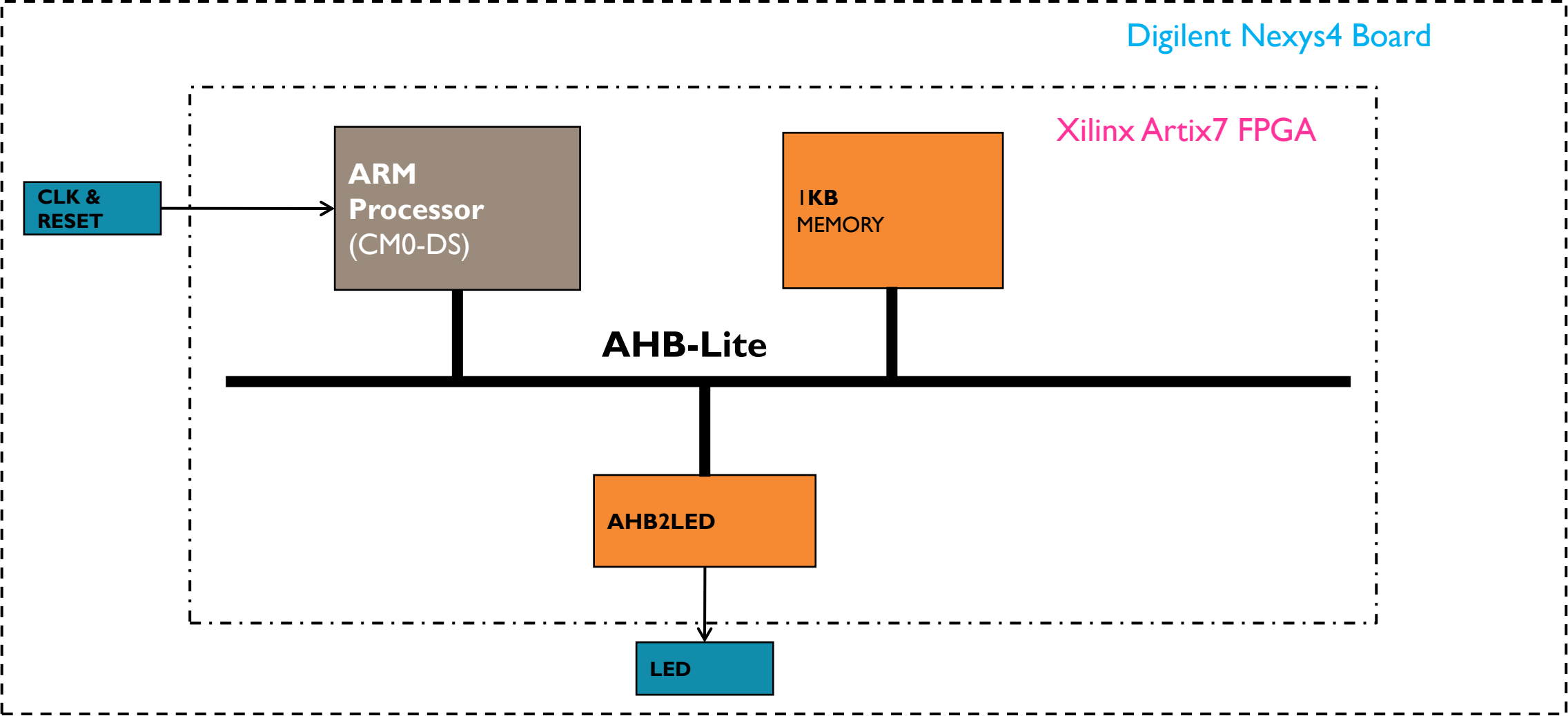


# Memory Map

	START ADDRESS	END ADDRESS	SIZE
MEM	0x0000_0000	0x00FF_FFFF	1KB (256 Words)
LED	0x5000_0000	0x50FF_FFFF	16MB

# AHB-Lite Master

- CM0-DS in our case

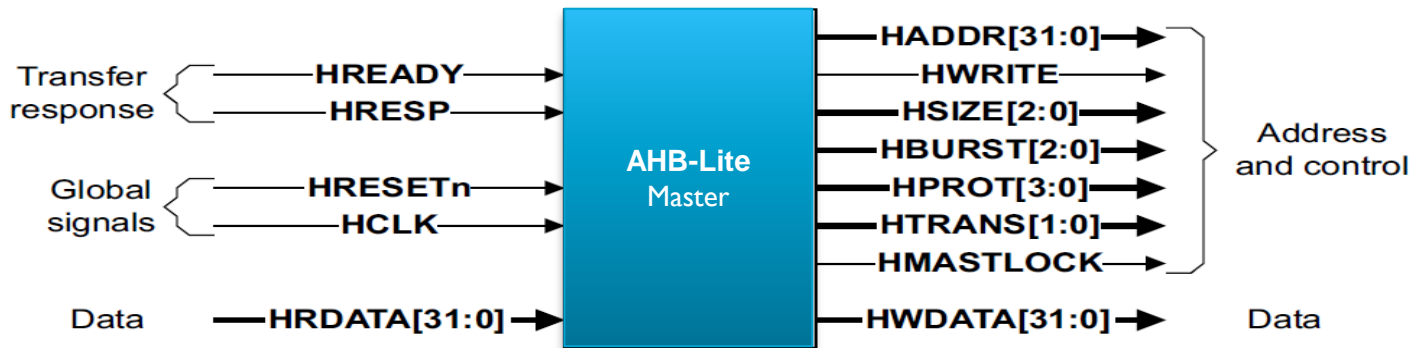


```
//AHBLite MASTER --> CM0-DS

CORTEXM0DS u_cortexm0ds (
    //Global Signals
    .HCLK          (HCLK),
    .HRESETn      (HRESETn),
    //Address, Control & Write Data
    .HADDR        (HADDR[31:0]),
    .HBURST       (HBURST[2:0]),
    .HMASTLOCK    (HMASTLOCK),
    .HPROT        (HPROT[3:0]),
    .HSIZE        (HSIZE[2:0]),
    .HTRANS       (HTRANS[1:0]),
    .HWDATA       (HWDATA[31:0]),
    .HWRITE       (HWRITE),
    //Transfer Response & Read Data
    .HRDATA       (HRDATA[31:0]),
    .HREADY       (HREADY),
    .HRESP        (HRESP),

    //CM0 Sideband Signals
    .NMI          (1'b0),
    .IRQ          (IRQ[15:0]),
    .TXEV         (),
    .RXEV         (1'b0),
    .LOCKUP       (LOCKUP),
    .SYSRESETREQ  (),
    .SLEEPING     ()
);
```
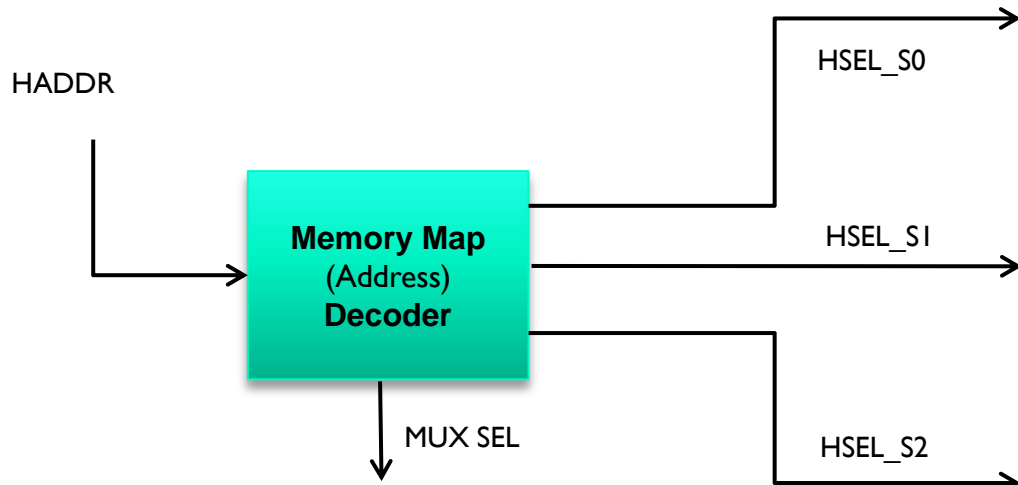
# Address Decoder

- **Combination Block**
- **Decodes the address of each transfer and provides a select signal for slave**
- **Provides control signal to Multiplexer**




```
//Address Decoder
AHBDCD uAHBDCD (
    .HADDR (HADDR[31:0]),

    .HSEL_S0 (HSEL_MEM),
    .HSEL_S1 (HSEL_LED),
    .HSEL_S2 (),
    .HSEL_S3 (),
    .HSEL_S4 (),
    .HSEL_S5 (),
    .HSEL_S6 (),
    .HSEL_S7 (),
    .HSEL_S8 (),
    .HSEL_S9 (),
    .HSEL_NOMAP (HSEL_NOMAP),

    .MUX_SEL (MUX_SEL[3:0])
);
```
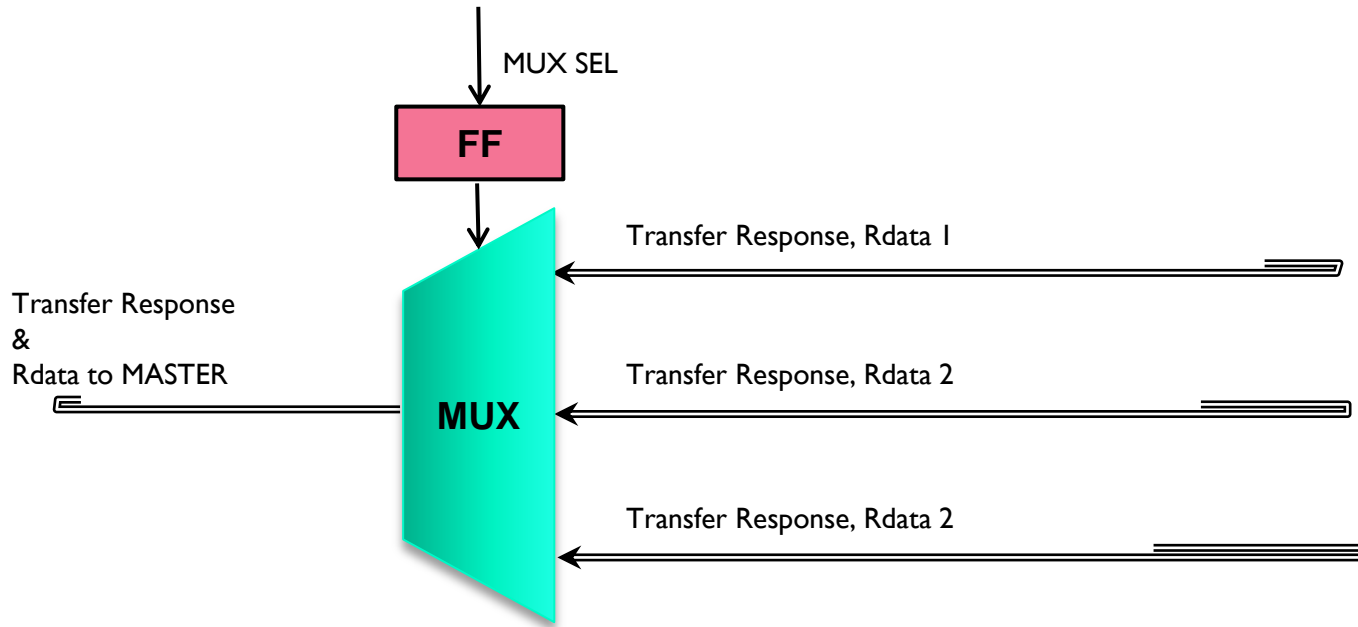
# Slave-to-Master Multiplexer

- **Multiplex the read data bus and response signals**
- **Decoder provides control (MUX\_SEL)**
- **Remember Pipelined Operation**




```
//Slave to Master Multitplexor
AHBMUX uAHBMUX (
    .HCLK (HCLK) ,
    .HRESETn (HRESETn) ,|
    .MUX_SEL (MUX_SEL[3:0]) ,

    .HRDATA_S0 (HRDATA_MEM) ,
    .HRDATA_S1 (HRDATA_LED) ,
    .HRDATA_S2 () ,
    .HRDATA_S3 () ,
    .HRDATA_S4 () ,
    .HRDATA_S5 () ,
    .HRDATA_S6 () ,
    .HRDATA_S7 () ,
    .HRDATA_S8 () ,
    .HRDATA_S9 () ,
    .HRDATA_NOMAP (32'hDEADBEEF) ,

    .HREADYOUT_S0 (HREADYOUT_MEM) ,
    .HREADYOUT_S1 (HREADYOUT_LED) ,
    .HREADYOUT_S2 (1'b1) ,
    .HREADYOUT_S3 (1'b1) ,
    .HREADYOUT_S4 (1'b1) ,
    .HREADYOUT_S5 (1'b1) ,
    .HREADYOUT_S6 (1'b1) ,
    .HREADYOUT_S7 (1'b1) ,
    .HREADYOUT_S8 (1'b1) ,
    .HREADYOUT_S9 (1'b1) ,
    .HREADYOUT_NOMAP (1'b1) ,

    .HRDATA (HRDATA[31:0]) ,
    .HREADY (HREADY)
) ;
```

# AHB Slaves

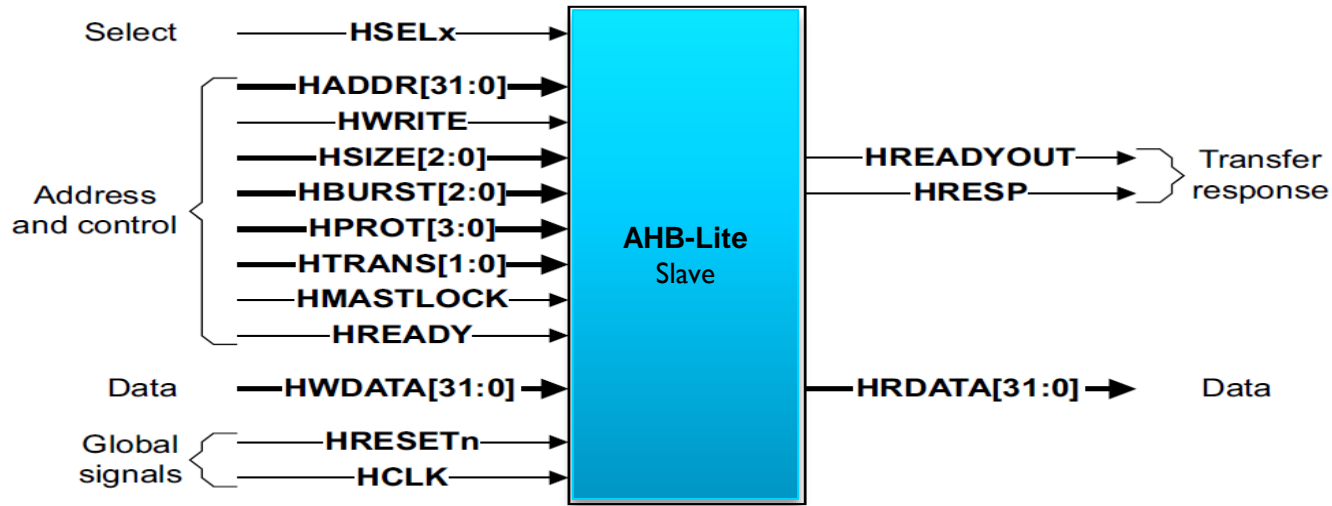

```
//AHBLite Slave
AHB2MEM uAHB2MEM (
    //AHBLITE Signals
    .HSEL (HSEL_MEM),
    .HCLK (HCLK),
    .HRESETn (HRESETn),
    .HREADY (HREADY),
    .HADDR (HADDR),
    .HTRANS (HTRANS [1:0]),
    .HWRITE (HWRITE),
    .HSIZE (HSIZE),
    .HWDATA (HWDATA [31:0]),

    .HRDATA (HRDATA_MEM),
    .HREADYOUT (HREADYOUT_MEM),
    //Sideband Signals
    .LED ()
);
```

```
//AHBLite Slave
AHB2LED uAHB2LED (
    //AHBLITE Signals
    .HSEL (HSEL_LED),
    .HCLK (HCLK),
    .HRESETn (HRESETn),
    .HREADY (HREADY),
    .HADDR (HADDR),
    .HTRANS (HTRANS [1:0]),
    .HWRITE (HWRITE),
    .HSIZE (HSIZE),
    .HWDATA (HWDATA [31:0]),


    .HRDATA (HRDATA_LED),
    .HREADYOUT (HREADYOUT_LED),
    //Sideband Signals
    .LED (LED [6:0])
);
```



# LAB Part I: Simulate the design and view AHB-Lite Transactions

1. Open “CODE” KEIL project in Lab Part I/Software folder and compile the design
2. Check code.hex gets generated
3. Copy your downloaded CM0-DS design files (CORTEXM0DS.v and cortexm0ds\_logic.v) to the “Lab Part I/FPGA/Source folder”
4. Follow Step 1 and Step 2 in the lab manual to simulate the design using Vivado design flow
5. Once the design starts simulation add these signals into the waveform from u\_cortexm0ds design instance
  1. AHB-Lite Signals
  2. Core register signals

# View AHB-Lite Transactions

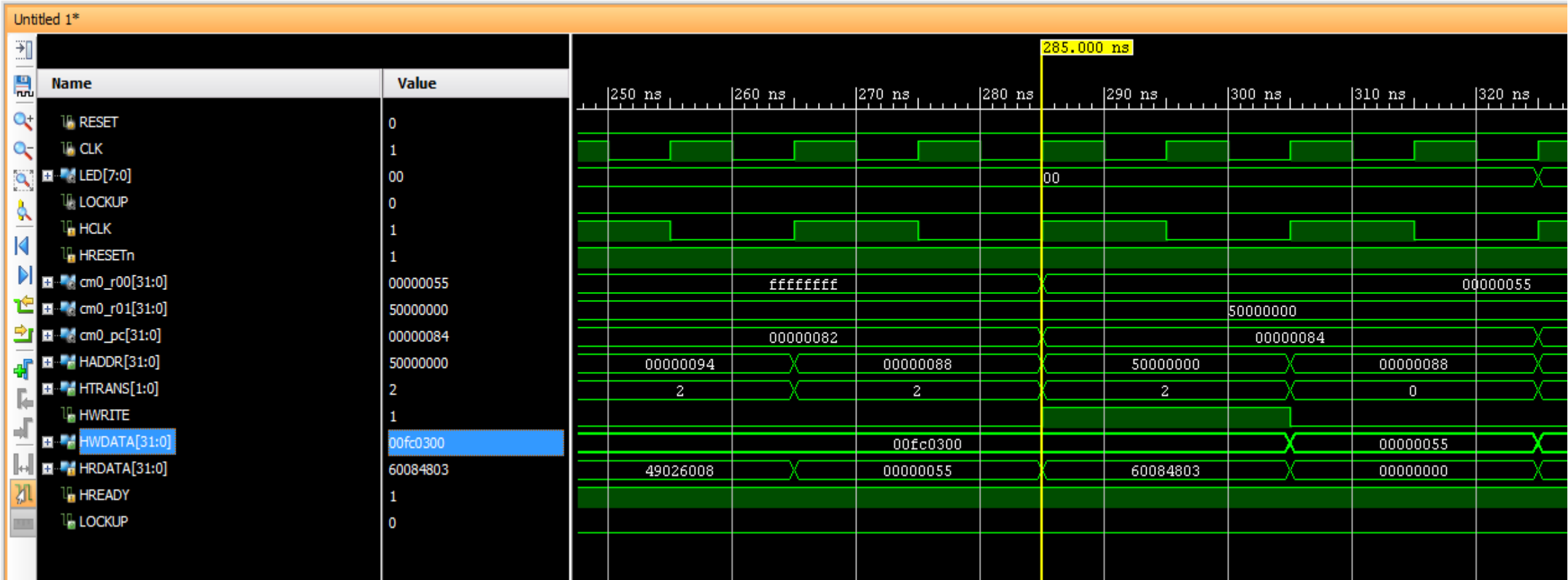

Read Transaction



Write Transaction

## LAB Part 2: Make those LEDs blink on the board!

1. Open “CODE” KEIL project in Lab Part2/Software folder and compile the design
2. Check code.hex gets generated
3. Copy your downloaded CM0-DS design files (CORTEXM0DS.v and cortexm0ds\_logic.v) to the “Lab Part2/FPGA/Source folder”
4. Open Vivado Project “Nexys4” inside “Lab Part2/FPGA/Nexys4 folder”
5. Follow Step 3, Step 4 and Step 5 in the lab manual to synthesize, implement and download the design on the board

# Result

