

SEMESTER 1 EXAMINATIONS 2003/04

INTEGRATED CIRCUIT DESIGN


Duration: 120 min

Answer THREE out of FIVE questions.

Calculators MAY be used, but not ones with text storage facilities.

Coloured pencils will be provided.

 
1. The Pull Up Networks (PUNs) for three static CMOS complementary gates are shown below:



For EACH gate:

- Derive a Boolean expression for the gate. (6 marks)
- Design a suitable Pull Down Network (PDN) to complete the gate. (6 marks)
- Find an Euler path for the gate if such a path exists.
Note that you may need to re-arrange the transistors within the schematic in order to find an Euler path. (10 marks)
- Derive a suitable stick diagram for efficient layout of the gate using a CMOS process supporting only one metal layer. (11 marks)

2. (a)

 

By drawing sub-circuit schematics (or otherwise), calculate the number of transistors in the above edge triggered D-type flip flop.

(4 marks)

(b) A transparent latch may be built around a multiplexer based on either transmission gates or tristate inverters.


With reference to an appropriate circuit diagram, show that we can build a master slave D-type using two such latches which will have fewer transistors than the edge triggered D-type from part (a).

(8 marks)

(c) Derive a stick diagram for the layout of your chosen master slave D-type.

(12 marks)

 (d) Discuss the operation of a D-type based on a *jamb latch* circuit such as shown below:



What are the benefits and drawbacks of this approach?

(9 marks)

TURN OVER

This page should be replaced with a page from the word file.

This page should be replaced with a page from the word file.


This page should be replaced with a page from the word file.

This page should be replaced with a page from the word file.

5. (a) Assume a symmetrical inverter CMOS design as reference, where $(W/L)_n=1/0.5$, $(W/L)_p=3/0.5$.

(i) Sketch the transistor level schematic of a 4-input (a,b,c,d) AND gate. Estimate the silicon area of the gate. (6 marks)

 (ii) An alternative implementation of a 4-input (a,b,c,d) AND gate is shown below:



Estimate the silicon area of this design.

(6 marks)

(iii) Compare the area and speed performance of the above two implementations of the 4-input AND gate.

(5 marks)

(b) (i) Derive a stick diagram for the layout of the 4-input AND gate designed in part (a)(i).

The layout should be suitable for use as a standard cell for a CMOS process that supports three metal layers.

(5 marks)

(ii) Draw a *black box* or *abstract* view of this gate as it might be supplied to an ASIC designer.

What other information is normally supplied with the *abstract* view to help the designer make use of the gate?

(4 marks)

(iii) Discuss with the aid of appropriate figures, the process of constructing a multi-cell layout based on these *abstract* views for a CMOS process that supports three metal layers.

(7 marks)