

SEMESTER 1 EXAMINATIONS 2008/09

INTEGRATED CIRCUIT DESIGN

Duration: 120 min

---

*Answer THREE out of FIVE questions.*

*University approved calculators MAY be used.*


*Coloured pens/pencils will be required.*

*Design rules for a sample CMOS process will be provided.*

*Graph paper will be available.*

 1.

The following circuit is to be implemented in static CMOS logic



(a) Derive a *stick diagram* for the implementation of each of the following basic gates

- (i) inverter
- (i) 2 input NAND gate
- (ii) 3 input NAND gate

Your designs should be suitable for use as standard cells for a CMOS process which supports multiple metal layers (please state whether your design is aimed at a two metal layer process or a three metal layer process).

(9 marks)

(b) Explain the purpose of a *black box* or *abstract* view in the standard cell design process. Illustrate your answer with abstract views for each of the standard cells you have designed.

(5 marks)

(c) Derive a stick diagram for the full circuit above based on the abstract views you have drawn.

(5 marks)

(d) Derive a boolean equation for Y in terms of A, B, C, D and E. Hence or otherwise derive a stick diagram for an alternative static CMOS implementation of this equation which uses fewer transistors.

(14 marks)



3.

(a) For each of the following logic families draw a *transistor level circuit diagram* of a 3 input NOR gate and briefly describe its operation:

- (i) Resistor Transistor Logic (RTL)
- (ii) NMOS Logic
- (iii) Static CMOS Logic

What are the advantages of CMOS for VLSI design compared to the older RTL and NMOS technologies.

(9 marks)

(b) Draw a *transistor level circuit diagram* for a 3 input NOR gate using pseudo-NMOS logic and briefly explain its operation. Discuss the usefulness of pseudo-NMOS NOR gates within a CMOS system design.

(7 marks)

(c) Realize the following logic functions using CPL logic:

- (i) AND/NAND
- (ii) OR/NOR

(4 marks)

Explain the general principle of operation of a dynamic logic inverter designed in pull-down topology.

(4 marks)

What are the advantages and disadvantages of a dynamic logic circuit? Explain with circuit diagrams (wherever appropriate) how can the disadvantages be handled?

(9 marks)