



- Bipolar Transistors with Resistors - MSI/LSI
  - RTL - NOR
  - TTL - NAND
  - ECS - OR/NOR

- MOS Transistors (no resistors) - VLSI
  - NMOS
  - CMOS - No static power!

*Both allow construction of NOR, NAND & Compound gate (always inverting)*