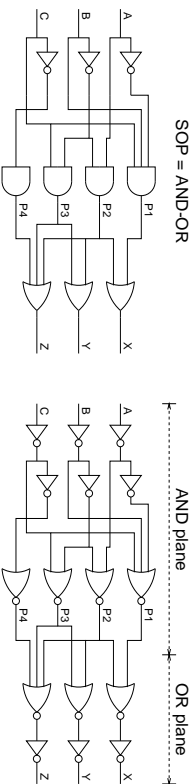


## PLAs, ROMs and RAMs

### PLA structures

Programmable Logic Array structures provide a logical and compact method of implementing multiple SOP (Sum of Products) or POS (Sum of Products) expressions.




Most PLA structures employ pseudo-NMOS NOR gates using a P-channel device in place of the NMOS depletion load.

9001

## PLAs, ROMs and RAMs

### Pseudo-NMOS NOR gate

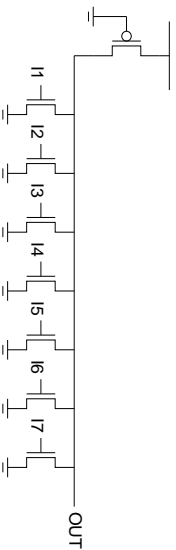


- Unlike complementary CMOS circuits, these gates will dissipate power under static conditions (since the P device is always on).
- The P and N channel devices must be ratioed in order to create the required low output voltage.
- This ratioing results in a slower gate, although there is a trade-off between gate speed and static power dissipation.

9002

## PLAs, ROMs and RAMs

### PLA structure

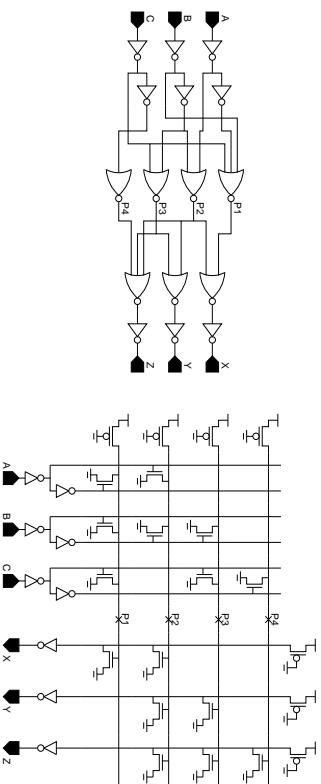


- A regular layout is employed, with columns for inputs and outputs and rows for intermediate expressions.

9003

## PLAs, ROMs and RAMs

### PLA structure

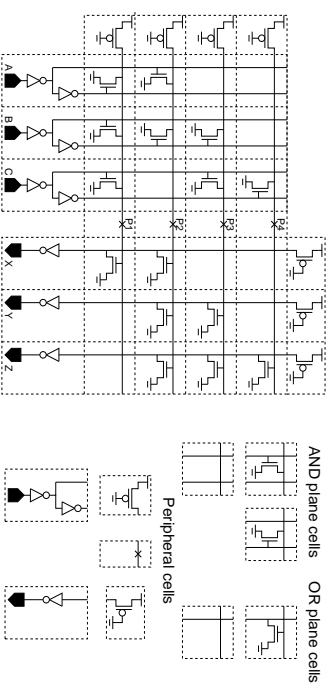


- Layout is simply a matter of selecting and placing rectangular cells from a limited set.

9004

## PLAs, ROMs and RAMs

### PLA structure

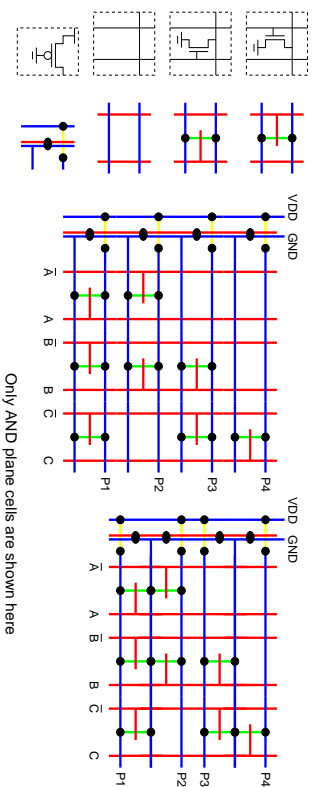


- Conversion to sticks is straight forward with opportunities for further optimization.

9005

## PLAs, ROMs and RAMs
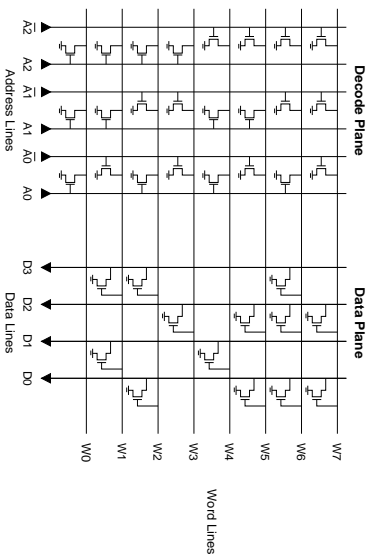
### ROMs

- A ROM may simply be a PLA with fixed decoder plane<sup>1</sup> and programmable data plane.




<sup>1</sup>RAM structures can make use of the same decode plane.

9006

## PLAs, ROMs and RAMs
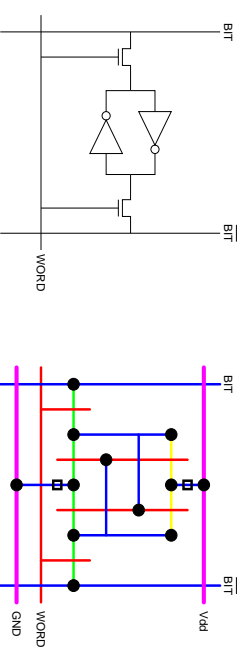
### Static RAM


- Used for high density storage on a standard CMOS process.
- Short lived conflict during write - NMOS transistors offer stronger path.
- Differential amplifiers are used for speedy read.



Standard 6 transistor static RAM cell.

9007

## SRAM Structure

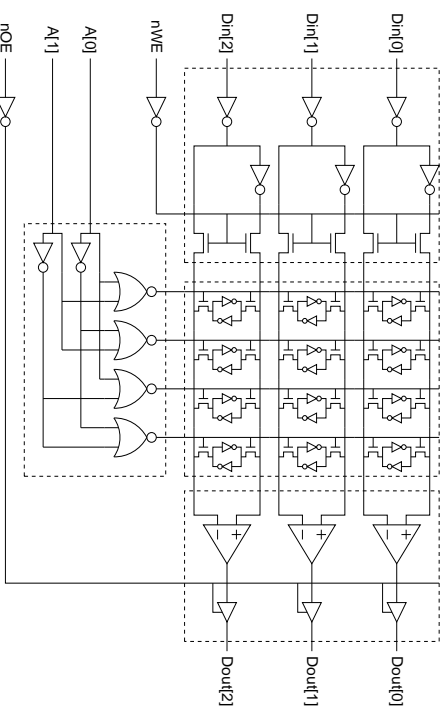

9008