

ICD.

Integrated Circuit Design

Iain McNally

≈ 12 lectures

Koushik Maharatna

≈ 12 lectures

1001

Integrated Circuit Design

Iain McNally

• Content

- Introduction
- Overview of Technologies
- Layout
- Design Rules and Abstraction
- Cell Design and Euler Paths
- System Design using Standard Cells
- Pass Transistor Circuits
- Storage
- PLAs
- Wider View

1002

Integrated Circuit Design

• Assessment

0% Informal Coursework (L-Edit Gate Layout)
100% Examination

• Books

Digital Integrated Circuits

Jan Rabaey
Prentice-Hall

Principles of CMOS VLSI Design

A Circuits and Systems Perspective

Neil Weste & David Harris
Addison-Wesley 2004

• Notes & Resources

<http://users.eecs.soton.ac.uk/bim/notes/icd>

1003

History

1947 First Transistor

John Bardeen, Walter Brattain, and William Shockley (Bell Labs)

1952 Integrated Circuits Proposed

Geoffrey Dummer (Royal Radar Establishment) - *prototype failed...*

1958 First Integrated Circuit

Jack Kilby (Texas Instruments) - *Co-inventor*

1959 First Planar Integrated Circuit

Robert Noyce (Fairchild) - *Co-inventor*

1961 First Commercial ICs

Simple logic functions from TI and Fairchild

1965 Moore's Law

Gordon Moore (Fairchild) observes the trends in integration.

1004

History

Moore's Law

Predicts exponential growth in the number of components per chip.

1965 - 1975 Doubling Every Year

In 1965 Gordon Moore observed that the number of components per chip had doubled every year since 1959 and predicted that the trend would continue through to 1975.

Moore describes his initial growth predictions as "ridiculously precise".

1975 - 2010 Doubling Every Two Years

In 1975 Moore revised growth predictions to doubling every two years.


Growth would now depend only on process improvements rather than on more efficient packing of components.

In 2000 he predicted that the growth would continue at the same rate for another 10-15 years before slowing due to physical limits.

1005

History

Moore's Law at Intel¹

 

¹Intel was founded by Gordon Moore and Robert Noyce from Fairchild

1006

History

Moore's Law; a Self-fulfilling Prophecy

The whole industry uses the Moore's Law curve to plan new fabrication facilities.

Slower - wasted investment

Must keep up with the Joneses².


Faster - too costly

Cost of capital equipment to build ICs doubles approximately every 4 years.




²or the Intels

1007

1947 Point Contact transistor

 


1961 Fairchild Bipolar RTL RS Flip-Flop

   


1965 Moore's Law (Mk I) Number of transistor has doubled every year and will continue to do so until 1975

 1975 Moore's Law (Mk II) Number of transistors will double every two years



Overview of Technologies


Components for Logic

 

2001

Overview of Technologies


RTL Inverter and NOR gate

 

2002

Overview of Technologies

 All functions can be realized with a single NOR base gate.¹




¹NAND gates could be used instead.

2003

Overview of Technologies

Other Bipolar Technologies

 


- **TTL** gives faster switching than RTL at the expense of greater complexity². The characteristic multi-emitter transistor reduces the overall component count.
- **ECL** is a very high speed, high power, non-saturating technology.

²Most TTL families are more complex than the basic version shown here

2004

Overview of Technologies

NMOS - a VLSI technology.

 


- Circuit function determined by series/parallel combination of devices.
- Depletion transistor acts as non-linear load resistor. Resistance increases as the enhancement device turns on, thus reducing power consumption.
- The low output voltage is determined by the size ratio of the devices.

2005

Overview of Technologies

CMOS logic

CMOS - state of the art VLSI.

 


- An active PMOS device complements the NMOS device giving:
 - rail to rail output swing.
 - negligible static power consumption.

2006

Digital CMOS Circuits

 Alternative representations for CMOS transistors




Various shorthands are used for simplifying CMOS circuit diagrams.

- In general substrate connections are not drawn where they connect to Vdd (PMOS) and Gnd (NMOS).
- All CMOS devices are enhancement mode.
- Transistors act as simple digitally controlled switches.

2007

Digital CMOS Circuits

Static CMOS complementary gates

 


- For any set of inputs there will exist either a path to Vdd or a path to Gnd.

2008

Digital CMOS Circuits

Compound Gates

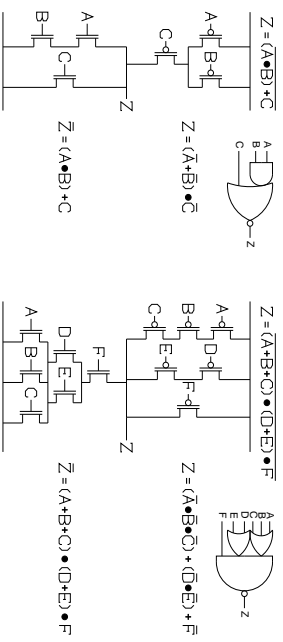

- All compound gates are inverting.
- Realisable functions are arbitrary AND/OR expressions with inverted output.

2009

Digital CMOS Circuits

Compound Gate Example

$$Z = \overline{(A \bullet B) + (C \bullet D)}$$

Pull Up Network



$$Z = f(\overline{A}, \overline{B}, \overline{C}, \overline{D})$$

$$Z = \dots$$












Pull Down Network

$$\overline{Z} = f(A, B, C, D)$$

$$\overline{Z} = (A \bullet B) + (C \bullet D)$$



2010

         

- Bipolar Transistors with Resistors - MSI/LSI

RTL - NOR

TTL - NAND

ECS - OR/NOR


- MOS Transistors (no resistors) - VLSI

NMOS

CMOS - No static power!


Both allow construction of NOR, NAND & Compound gate (always inverting)

Photolithography

 

4001

Mask Making

 


- Optical reduction allows narrower line widths.

4002


Design Rules

To prevent chip failure, designs must conform to design rules:

- Single layer rules

 


- Multi-layer rules

 

4003


Derivation of Design Rules

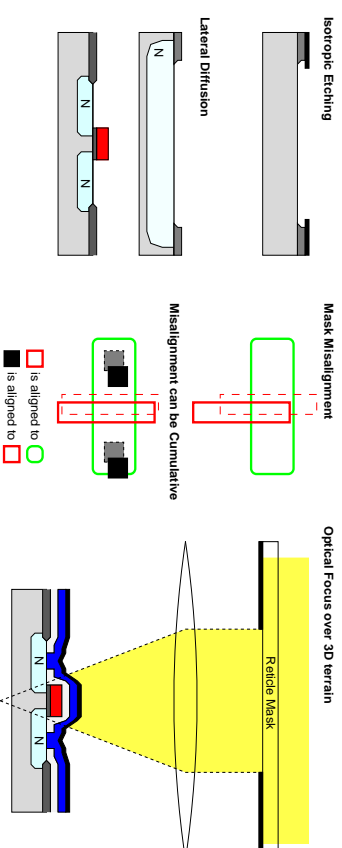

4004

Design Rules


0.5 μm CMOS inverter

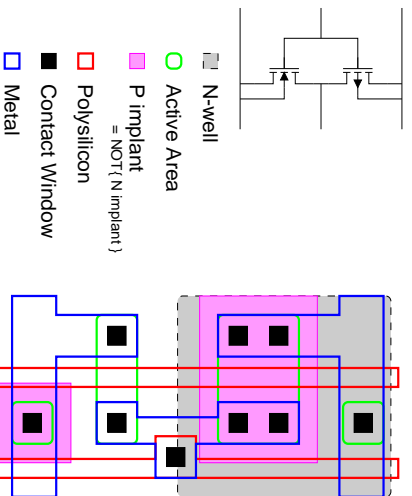

4005

Abstraction


Levels of Abstraction

 

- Mask Level Design
 - Laborious Technology-/Process dependent.
 - Design rules may change during a design!
- Transistor Level Design
 - Process independent, Technology dependent.
- Gate Level Design
 - Process/Technology independent.

4006

Abstraction - Stick Diagrams

 

Stick diagrams give us many of the benefits of abstraction:

- Much easier/faster than full mask specification.
- Process independent (valid for any CMOS process).
- Easy to change.

while avoiding some of the problems:


- Optimized layout may be generated much more easily from a stick diagram than from transistor or gate level designs.¹

¹note that all IC designs must end at the mask level.

4007


Digital CMOS Design

Stick Diagrams

 

4008

Stick Diagrams

 


4009

Stick Diagrams


- *Explore your Design Space.*
 - Implications of crossovers.
 - Number of contacts.
 - Arrangement of devices and connections.
- Process independent layout.
- Easy to expand to a full layout for a particular process.

4010

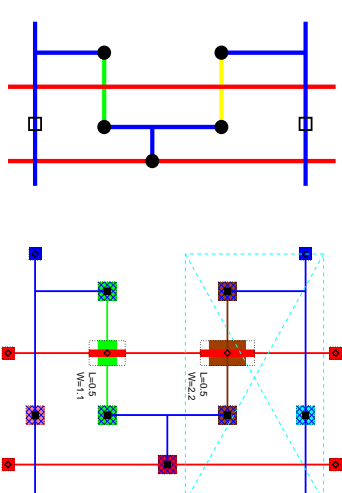

- Transistors are placed and explicitly sized.
 - components are joined with zero width wires.
 - contacts are automatically selected as required.
- A semi-automatic compaction process will create DRC correct layout.


4011

 


- Log style design (sticks with width) - DRC errors are flagged immediately.
 - again contacts are automatically selected as required.
- On-line DRC leads to rapid generation of correct designs.
 - symbolic capture style compaction is available if desired.

4012


Processing

 

 
Design Rules - width, separation, overlap



Optimised Mask Layout

 

Equivalent Stick Diagram

 


- Metal
- Polysilicon
- N+
- P+
- Contact
- Tap
- Combined contact & tap

Digital CMOS Design

A logical approach to gate layout.

 - All complementary gates may be designed using a single row of n-transistors above or below a single row of p-transistors, aligned at common gate connections.




5001

Digital CMOS Design

Euler Path

 - For the majority of these gates we can find an arrangement of transistors such that we can butt adjoining transistors.
 - Careful selection of transistor ordering.
 - Careful orientation of transistor source and drain.
- Referred to as *line of diffusion*.



5002

Digital CMOS Design

Finding an Euler Path

Computer Algorithms

- It is relatively easy for a computer to consider all possible arrangements of transistors in search of a suitable Euler path. This is not so easy for the human designer.




One Human Algorithm

- Find a path which passes through all n-transistors exactly once.
- Express the path in terms of the gate connections.
- Is it possible to follow a similarly labelled path through the p-transistors?
 - Yes – you've succeeded.
 - No – try again (you may like to try a p path first this time).

5003

Digital CMOS Design


Finding an Euler Path

   

Here there are four possible Euler paths.


5004

Finding an Euler Path

 

5005

Euler Path Example

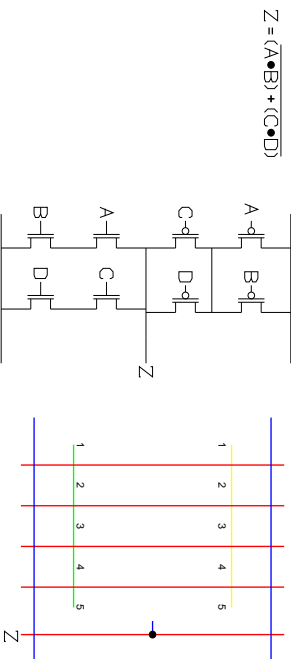


1. Find Euler path
 2. Label poly columns
 3. Route power nodes
 4. Route output node
 5. Route remaining nodes
 6. Add taps¹ for PMOS and NMOS
- A combined contact and tap, ■, may be used only where a power contact exists at the end of a line of diffusion. Where this is not the case a simple tap, —■, should be used.

¹ Tap is good for about 6 transistors – insufficient taps may leave a chip vulnerable to latch-up

5006


Finding an Euler Path

 

No possible path through n-transistors!

5007



Finding an Euler Path

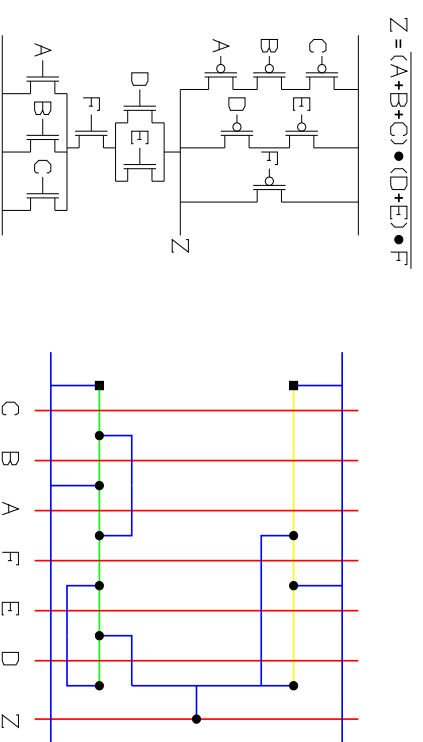

5008



Finding an Euler Path
  
$$Z = (A+(D \bullet E)) \bullet (B+(F \bullet G)) \bullet (C+(H \bullet I))$$



No possible path through P-transistors.
 No re-arrangement will create a solution!

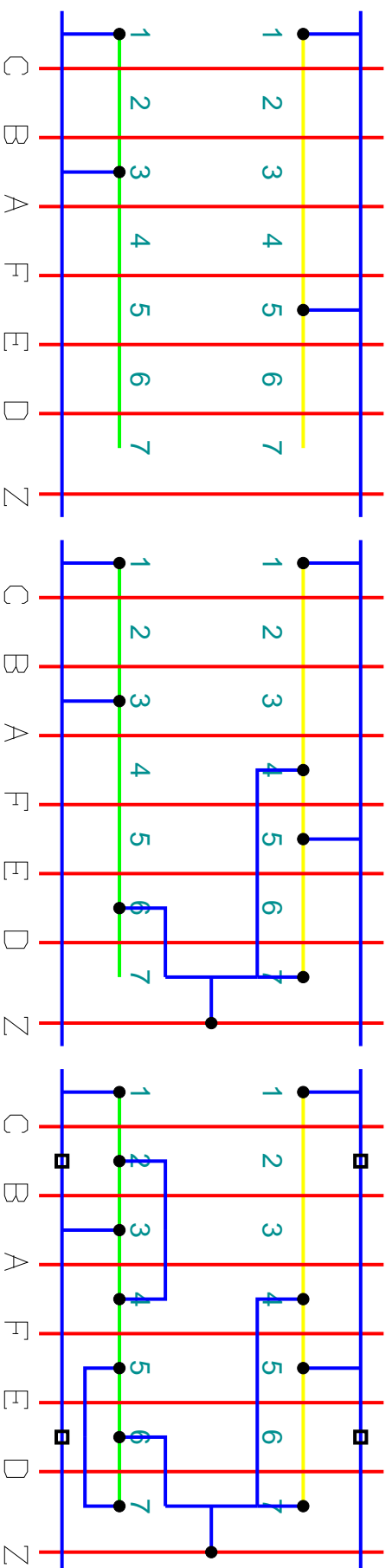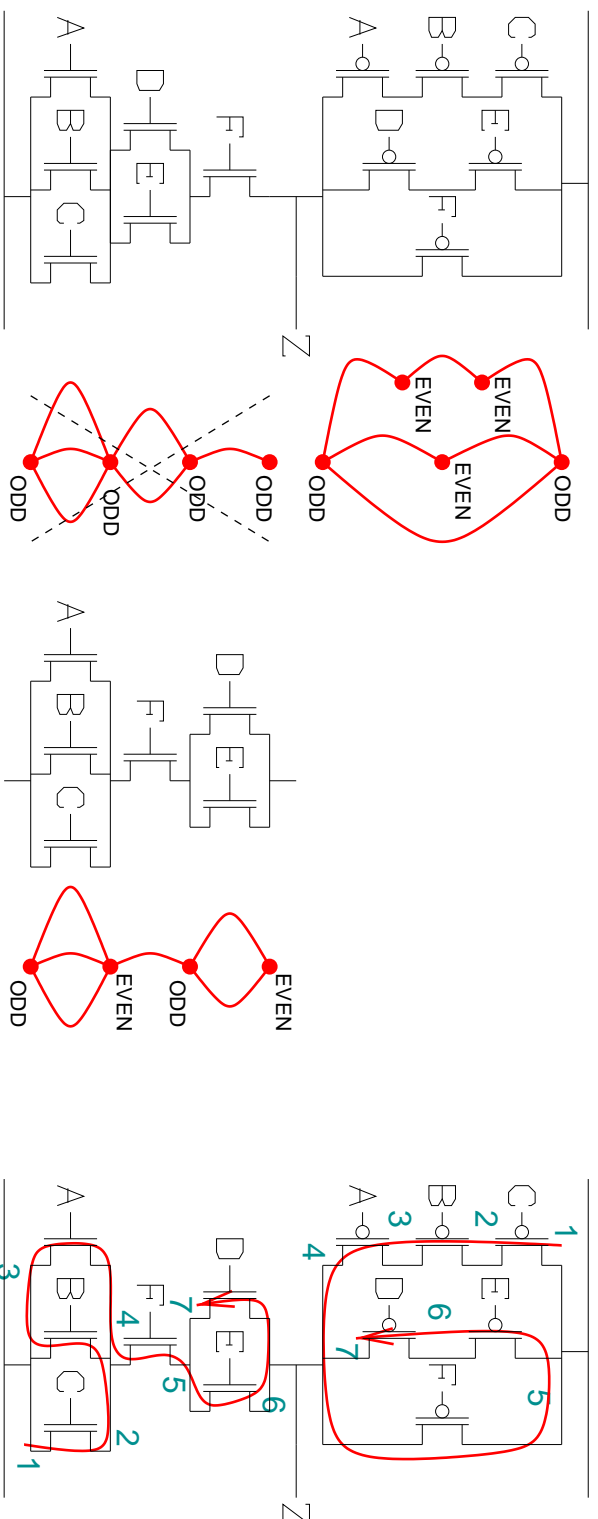
Investigation of Euler paths leads to more efficient layout*



*not all gates will support a common Euler path for both PMOS and NMOS

5000

Multiple gates

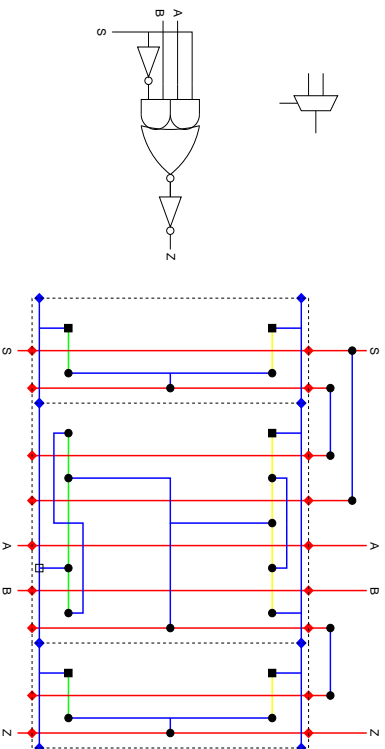


6001

Multiple gates

- Gates should all be of same height.
 - Power and ground rails will line up when butted.
- All gate inputs and outputs are available at top and bottom.
 - All routing is external to cells.
 - Preserves the benefits of hierarchy.
- Interconnect is via *two conductor routing*.
 - In this case Polysilicon vertically and Metal horizontally.

6002

Two-layer Metal

 

Most modern VLSI processes support two or more metal layers. The norm is to use only metal for inter-cell routing. Usually Metal1 horizontally (and for power rails) and Metal2 vertically (and for cell inputs and outputs).

6003

Many ICs are designed using the standard cell method.


- Cell Library Creation
 - A cell library, containing commonly used logic gates, is created for a process. This is often carried out by or on behalf of the foundry.
- ASIC¹ Design
 - The ASIC designer must design a circuit using the logic gates available in the library.
 - The ASIC designer usually has no access to the full layout of the standard cells and doesn't create any new cells for the library.
 - Layout work performed by the ASIC designer is divided into two stages:
 - Placement
 - Routing

¹Application Specific Integrated Circuit

6004

Placement & Routing

Placement

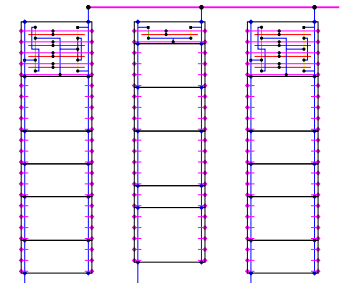

Cells are placed in one or several equal length lines with inter-digitated power and ground rails.

6005

Placement & Routing

Two conductor routing


- This logical approach means that we should never have to worry about signals crossing.
- This makes life considerably easier for a computer (or even a human) to complete the routing.
- We must only ensure that two signals will not meet in the same horizontal or vertical channel.
- Computer algorithms can be used to ensure placement of cells such that wires are short.²
- Further computer algorithms can be used to optimize the routing itself.

²In VLSI circuits we often find that inter-cell wiring occupies more area than the cells themselves.

6007

Placement & Routing

Routing

 

In the routing channels between the cells we route metal1 horizontally and metal2 vertically.



6006

Standard Cell Design


More Metal Layers

With three or more metal layers it is possible to take a different approach. The simplest example uses three metal layers.

  - Standard Cells
- Use only metal1 except for I/O which is in metal2
- Two Conductor Routing
- Uses metal2 and metal3




6008

 

Standard Cell Design

More Metal Layers

 


With this approach we can route safely over the cell to the specified pins leading to much smaller gaps between cell rows.

6009

Standard Cell Design

Alternative Placement Style

 

By flipping every second row it may be possible to eliminate gaps between rows. N-wells are merged and power or ground rails are shared. This approach is normally associated with sparse rows and non channel based routing algorithms.





6010

LAYOUT





ABSTRACT

ROUTING





1 METAL LAYER

  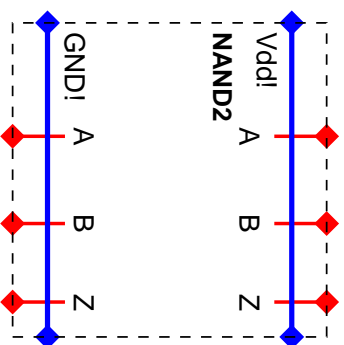 

2 METAL LAYERS

 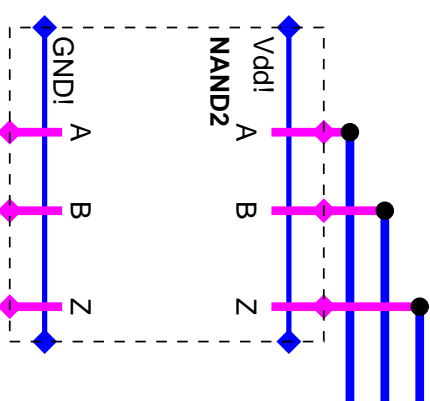  


3 METAL LAYERS

    

6000

Static CMOS Complementary Gates

 

- **Static**
After the appropriate propagation delay the output becomes valid and remains valid.¹

- **Complementary**


For any set of inputs there will exist either a path to Vdd or a path to GND. Where this condition is not met we have either a high impedance output or a conflict in which the strongest path succeeds. Static CMOS **Non-complementary** gates make use of these possibilities.

¹c.f. Dynamic logic which uses circuit capacitance to store state for a short time.

7001

Pass Transistor Circuits

- **Pass Transistor**

 

- Provides very compact circuits.
- Good transmission of logic '0'.
- Poor transmission of logic '1'.
- - slow rise time
- - degradation of logic value

The pass transistor is used in many dynamic CMOS circuits².


²where pull-up is performed by an alternative method

7002

Pass Transistor Circuits

- **Transmission Gate**

 - For static circuits we would normally use a CMOS transmission gates:




- - balanced n and p pass transistors
- - faster pull-up
- - slower pull-down

7003

Pass Transistor Circuits

- **Transmission Gate Layout**

 


- note that these circuits are not fully complementary³ hence they do not immediately lend themselves to a *line of diffusion* implementation.

³since there are sets of inputs for which the output is neither pulled low nor high

7004

Pass Transistor Circuits

• Transmission Gate Multiplexor

 


- very few transistors 4 (+2 for inverter)
- difficult layout may offset this advantage
- - prime candidate for 2 level metal

7005

Pass Transistor Circuits

• Bus Wiring

 


- distributed multiplexing⁴
- only one inverter required per bank of transmission gates
- greatly simplifies global wiring

⁴Internal chip bus should never be allowed to float high impedance

7006

Bus Distributed Multiplexing

 


Ideal for signals with many drivers from different modules.

7007

Bus Distributed Multiplexing

Implementation of bitslice ALU:⁵

 


- Separate circuit for each function
- Connected via distributed multiplexor

⁵Note that transmission gates have no drive capability in themselves. Here a good drive is ensured by providing buffers.

7008

Bus Distributed Multiplexing

 


- Single optimized ALU module
- Multiplexing is not distributed
- Multiplexor implementation may use transmission gates

7009

Pass Transistor Circuits

- Tristate Inverter

 


- Any gate may have a tri-state output by combining it with a transmission gate.

7010

Pass Transistor Circuits

- Tristate Inverter

 


- Alternatively the transmission gate may be incorporated into the gate.
 - - one connection is removed - easier to layout
 - - also easier to simulate!

7011

Pass Transistor Circuits


- Tristate Inverter Layout

 



7012

Pass Transistor Circuits


- Tristate Inverter Bus Driver

 

  - a tristate inverting buffer is often used to drive high capacitance bus signals
- transistors may be sized as required




Transmission Gate Multiplexor


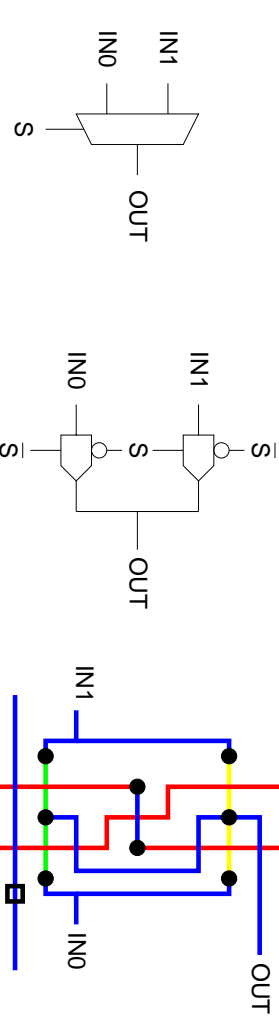


*note distinctive polysilicon crossover

Tri-state Inverter

 


Tri-state Buffer

  


Tri-state gates are used for Multiplexing


Distributed Multiplexing

 

using tri-state buffers

 


Bi-directional I/O

 

*this is another form of multiplexing

Latches and Flip-Flops

- CMOS transmission gate latch

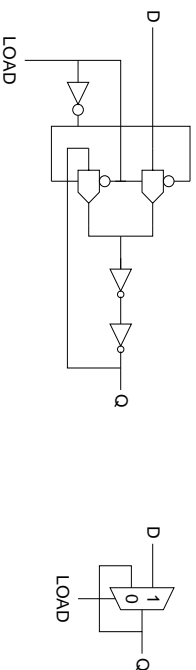


- A simple transparent latch can be build around a transmission gate multiplexor
- transparent when load is high
 - latched when load is low
 - two inverters are required since the transmission gate cannot drive itself

8001

Latches and Flip-Flops

- Transmission gate latch layout

 


- a compact layout is possible using 2 layer metal

8002

Latches and Flip-Flops

 - A simpler layout may be achieved using tristate inverters.




- this design requires two additional transistors but may well be more compact.

8003

Latches and Flip-Flops

 - For use in simple synchronous circuits we use a pair of latches in a master slave configuration.




- this avoids the race condition in which a transparent latch drives a second transparent latch operating on the same clock phase.
- the circuit behaves as a rising edge triggered D type flip-flop.


8004

Latches and Flip-Flops

- Transmission gate implementation

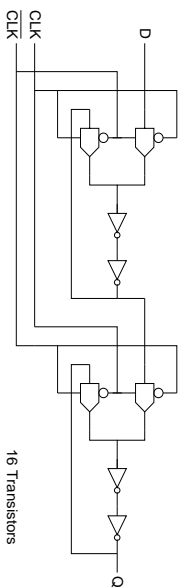


- Tristate inverter implementation

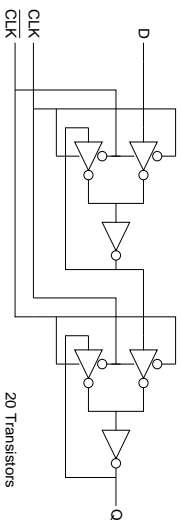


8005

Latches and Flip-Flops

- Alternative configuration

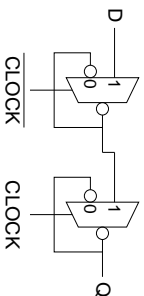


– Implementation

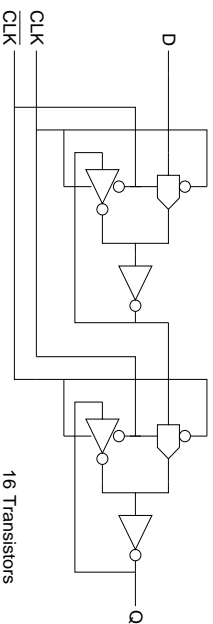


8006

Latches and Flip-Flops

- Layout of master slave D type.

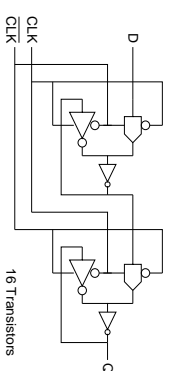

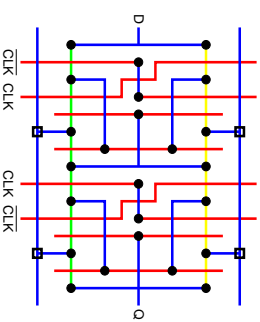
– very compact using alternative configuration.




8007

Latches and Flip-Flops

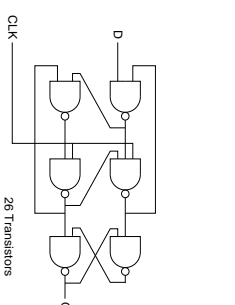- For the same functionality we could use an edge triggered D type:




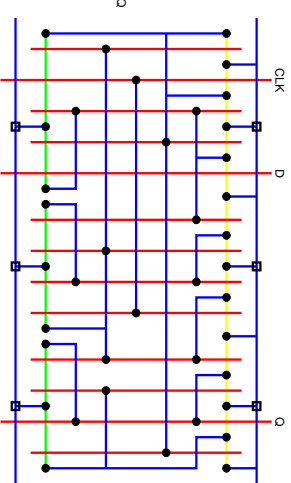
- a few more transistors
- more complex wiring
- simpler clock distribution



8008


Register File

  Where we have large amounts of storage the use of individual latches can lead to space saving.




- Load signals must be glitch free with tightly controlled timing.
- Edge Triggered D-type prevents a race condition ($Reg1 \leftarrow Reg1 + Reg2$).

Latch


 


Master Slave D-Type Flip-Flop

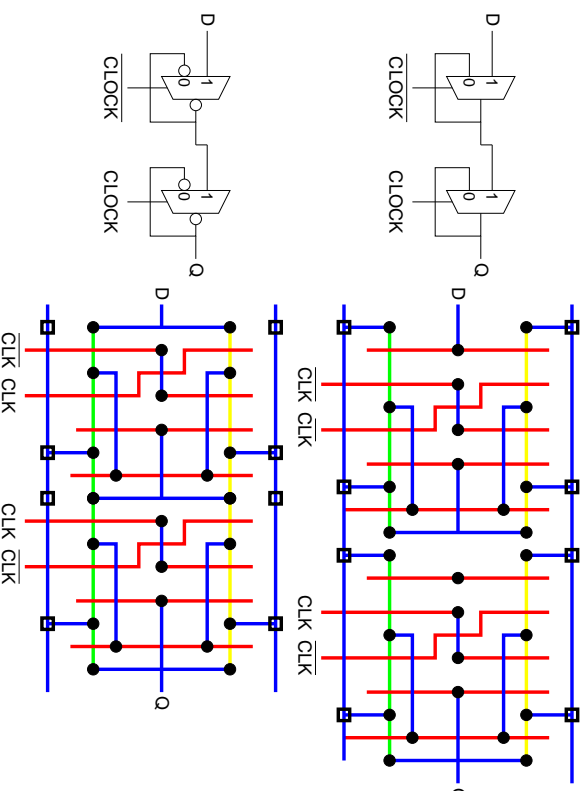

*multiplexor based latches and flip-flops include distinctive polysilicon crossover

Edge Triggered D-Type Flip-Flop

  


Euler path analysis is applied creatively to these multi-gate cells - gates are often linked via the common gnd/pwr node
 Final layouts will be more complex where clock buffers, reset circuitry and metal 2 i/o are included

PLAs, ROMs and RAMs

PLA structures

 Programmable Logic Array structures provide a logical and compact method of implementing multiple SOP (Sum of Products) or POS (Sum of Products) expressions.




Most PLA structures employ pseudo-NMOS NOR gates using a P-channel device in place of the NMOS depletion load.

9001

PLAs, ROMs and RAMs

Pseudo-NMOS NOR gate

 


- Unlike complementary CMOS circuits, these gates will dissipate power under static conditions (since the P device is always on).
- The P and N channel devices must be ratioed in order to create the required low output voltage.
- This ratioing results in a slower gate, although there is a trade-off between gate speed and static power dissipation.

9002

PLAs, ROMs and RAMs

PLA structure

 


- A regular layout is employed, with columns for inputs and outputs and rows for intermediate expressions.

9003

PLAs, ROMs and RAMs

PLA structure

 


- Layout is simply a matter of selecting and placing rectangular cells from a limited set.

9004

PLAs, ROMs and RAMs

PLA structure

 


- Conversion to *sticks* is straight forward with opportunities for further optimization.

9005

PLAs, ROMs and RAMs

ROMs

 - A ROM may simply be a PLA with fixed decoder plane¹ and programmable data plane.




¹RAM structures can make use of the same decode plane.

9006

PLAs, ROMs and RAMs

Static RAM

 
- Used for high density storage on a standard CMOS process.
- Short lived conflict during write - NMOS transistors offer stronger path.
- Differential amplifiers are used for speedy read.



Standard 6 transistor static RAM cell.


9007

SRAM Structure




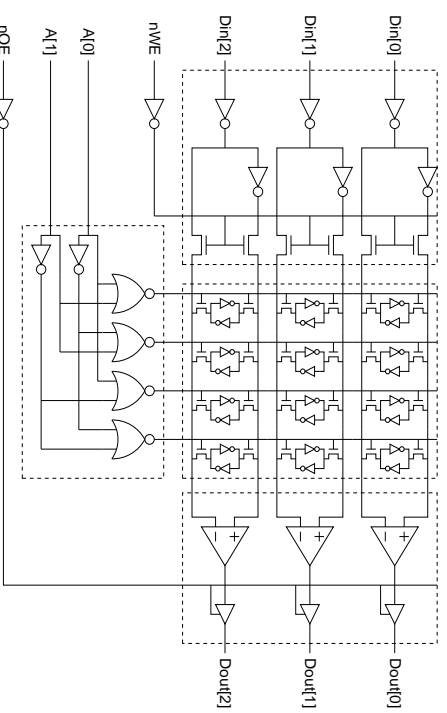


9008


PLA and ROM

 

SRAM

 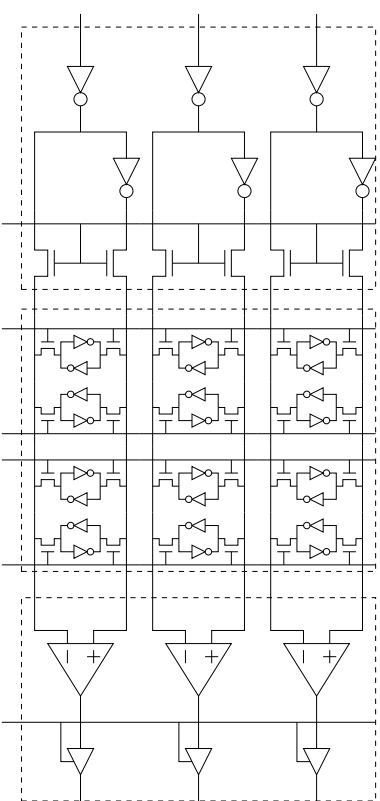  

 ROM is PLA with
fixed AND (decoder) plane
programmable OR (data) plane



Cells are designed to butt together in two dimensions leading to efficient layout

PLA layout efficiency will depend on the actual function implemented (e.g. number of common product terms)

System Design Choices

- Programmable Logic
 - PLD
 - e.g. PAL 22V10, ICT PEEL22CV10, Lattice ispGAL22V10
 - Field Programmable Gate Array (FPGA)
 - e.g. Xilinx XC4013, Altera Cyclone EP1C12
- Semi-Custom Design
 - Mask Programmable Gate Array
 - e.g. ECS CMOS Gate Array
 - Altera HardCopy II structured ASICs
 - Standard Cell Design
 - e.g. Alcatel Mietec MTC45000 0.35 μm cell library
- Full Custom Design

10001

System Design Choices


- Programmable Logic
 - Best possible design turnaround time
 - Cheapest for prototyping
 - Best time to market
 - Minimum skill required
- Semi-Custom Design
- Full Custom Design
 - Cheapest for mass production
 - Fastest
 - Lowest Power
 - Highest Density¹
 - Most skill required

START HERE

10002

¹Optimization limited by speed/power/area trade off


Programmable Logic

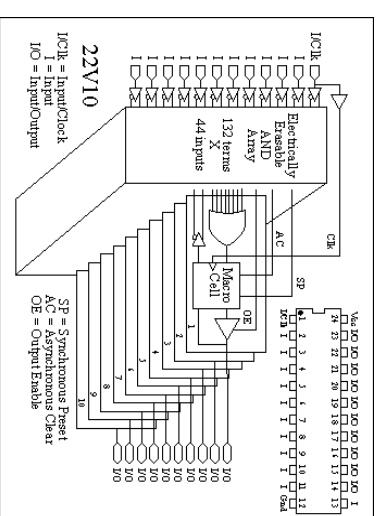

- One time use - Fuse programmable.
- Reprogrammable - UV/Electrically Erasable.

10003

 Field Programmable Gate Array - Xilinx XC4000




- Configurable Logic Blocks & I/O Blocks²
- Programmable Interconnect

10004

²Xilinx XC4013 has 576 (24 × 24) CLBs and up to 192 (4 × 48) user I/O pins.

 Field Programmable Gate Array – Altera Cyclone




- Logic Array Blocks, M4K Ram Blocks & I/O Elements³
- Programmable Interconnect

³Altera Cyclone EP1C12 has 12060 Logic Elements (arranged as 1206 Logic Array Blocks) and up to 249 user I/O pins.

10004

 
Field Programmable Gate Array – Xilinx XC4000 CLB



10005


Multiplexer Controlled by Configuration Program
36932

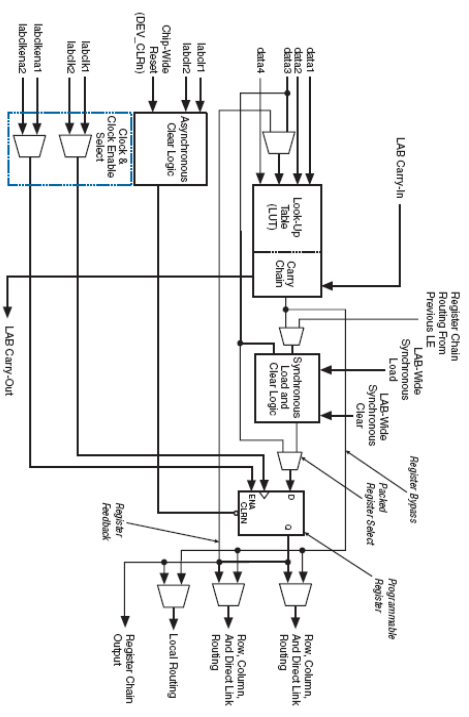Field Programmable Gate Array – Altera Cyclone LE




10005

Mask Programmable Gate Array

 

10006

Mask Programmable Gate Array

 


- Customize Metal and Contact Window masks only.

10007

Standard Cell Design

- Logic Functions

 

- Auto Generated Macro Blocks

- PLA
- ROM
- RAM

- System Level Blocks

- Microprocessor core⁴

⁴Will support System On Chip applications.

10008

Full Custom

All design styles need full custom designers

- to design the base programmable logic chips
- to design building blocks for semi-custom


Where large ASICs use full custom techniques they are likely to be used alongside semi-custom techniques.

e.g. Hand-held computer game chip

- Full custom bitslice datapath hand crafted for optimum area efficiency and low power consumption
- Standard cell controller
- Macro block RAM, ROM

10009

 Programmable Semi-Custom Full Custom
Logic



All design styles need full custom designers

A large ASIC (especially SoC) may mix Semi-Custom and Full Custom

10000