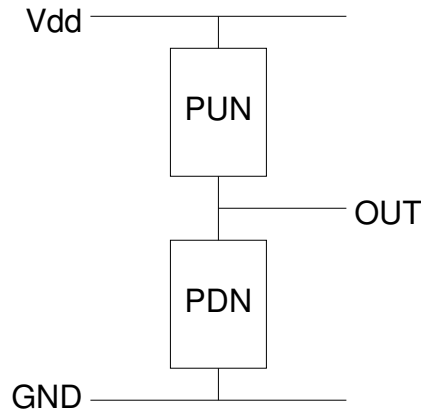


# Static CMOS Complementary Gates

---



- **Static**

After the appropriate propagation delay the output becomes valid and remains valid.<sup>1</sup>

- **Complementary**

For any set of inputs there will exist either a path to  $V_{dd}$  or a path to GND.

Where this condition is not met we have either a high impedance output or a conflict in which the strongest path succeeds. Static CMOS **Non-complementary** gates make use of these possibilities.


---

<sup>1</sup>c.f. Dynamic logic which uses circuit capacitance to store state for a short time.

# Pass Transistor Circuits

---

- Pass Transistor

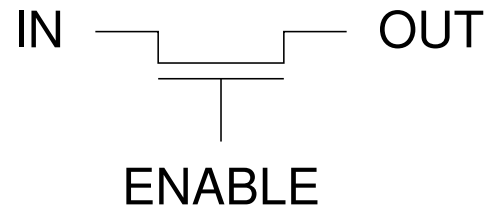

- Provides very compact circuits.
- Good transmission of logic '0'.
- Poor transmission of logic '1'.
  - - slow rise time
  - - degradation of logic value

The pass transistor is used in many dynamic CMOS circuits<sup>2</sup>.

---


<sup>2</sup>where pull-up is performed by an alternative method

# Pass Transistor Circuits

---

- Transmission Gate

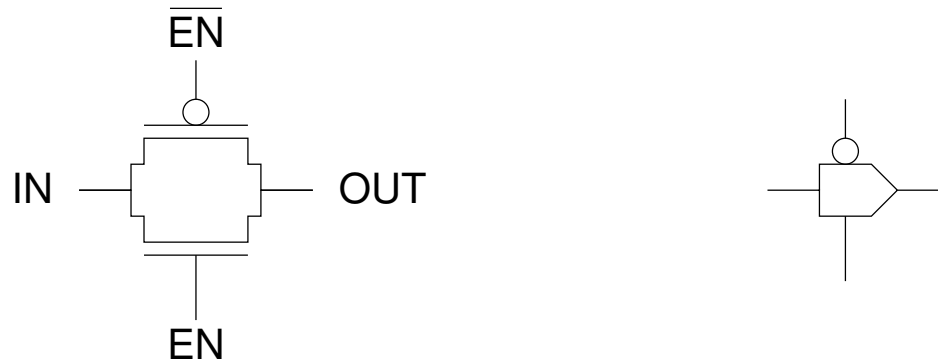- For static circuits we would normally use a CMOS transmission gates:




- - balanced  $n$  and  $p$  pass transistors
- - faster pull-up
- - slower pull-down

# Pass Transistor Circuits

---

- Transmission Gate Layout

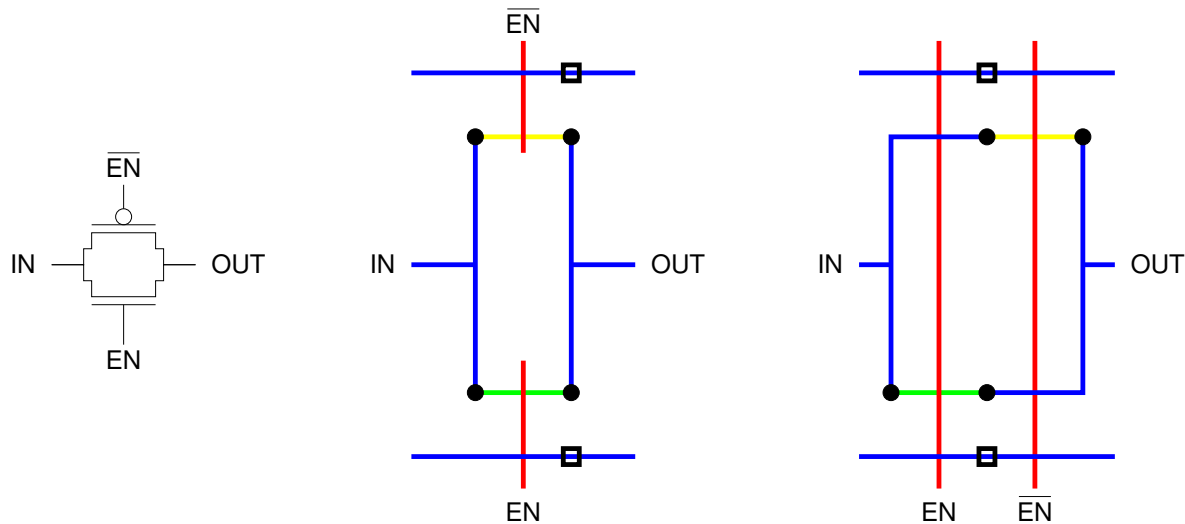

– note that these circuits are not fully complementary<sup>3</sup> hence they do not immediately lend themselves to a *line of diffusion* implementation.


---

<sup>3</sup>since there are sets of inputs for which the output is neither pulled low nor high

# Pass Transistor Circuits

---

- Transmission Gate Multiplexor

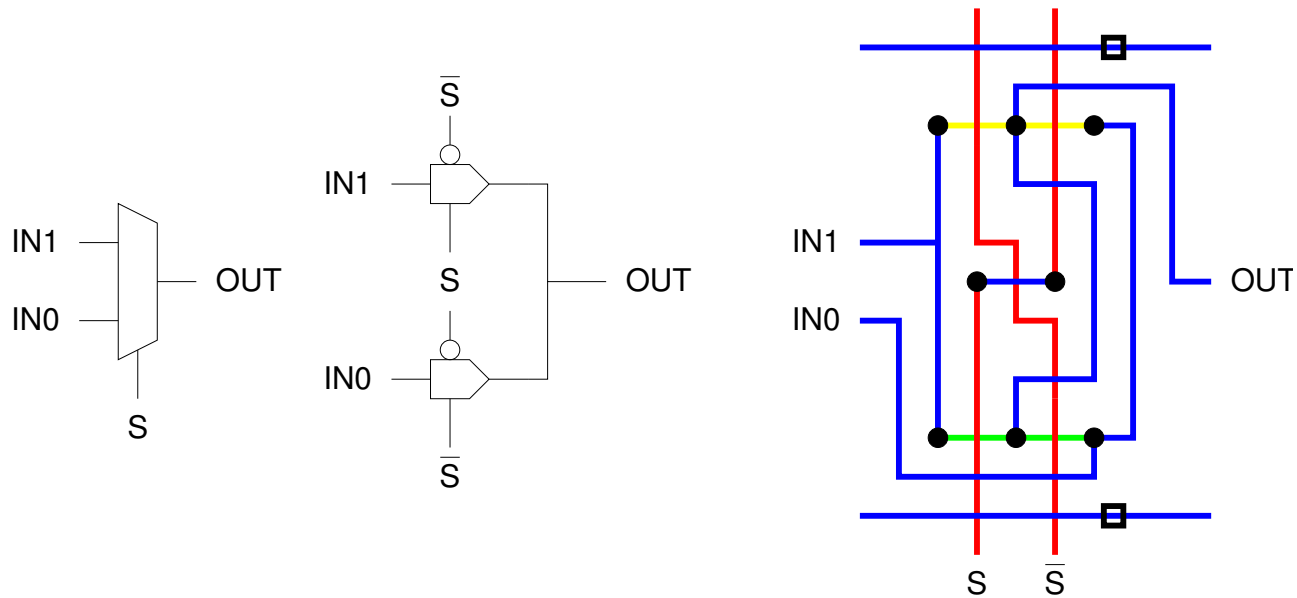


- very few transistors 4 (+2 for inverter)
- difficult layout may offset this advantage
  - - prime candidate for 2 level metal

# Pass Transistor Circuits

---

- Bus Wiring

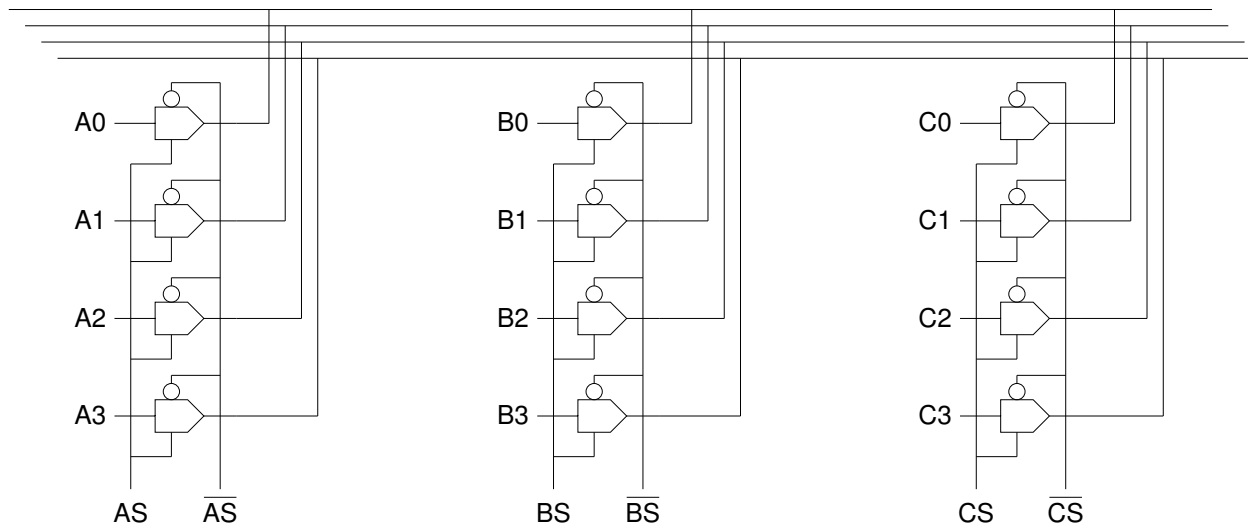


- distributed multiplexing<sup>4</sup>
- only one inverter required per bank of transmission gates
- greatly simplifies global wiring

---

<sup>4</sup>internal chip bus should never be allowed to float high impedance

# Bus Distributed Multiplexing


---

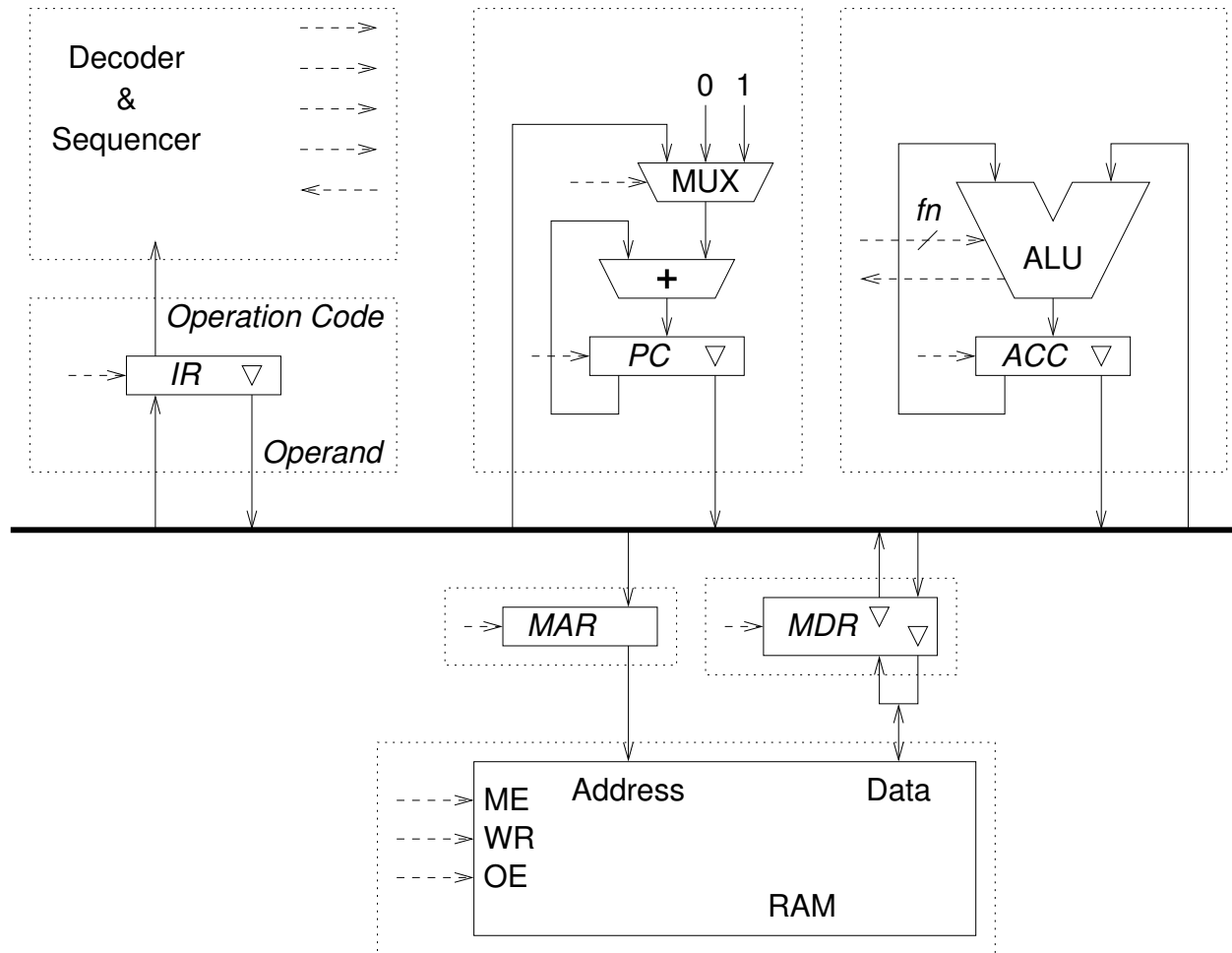

Ideal for signals with many drivers from different modules.
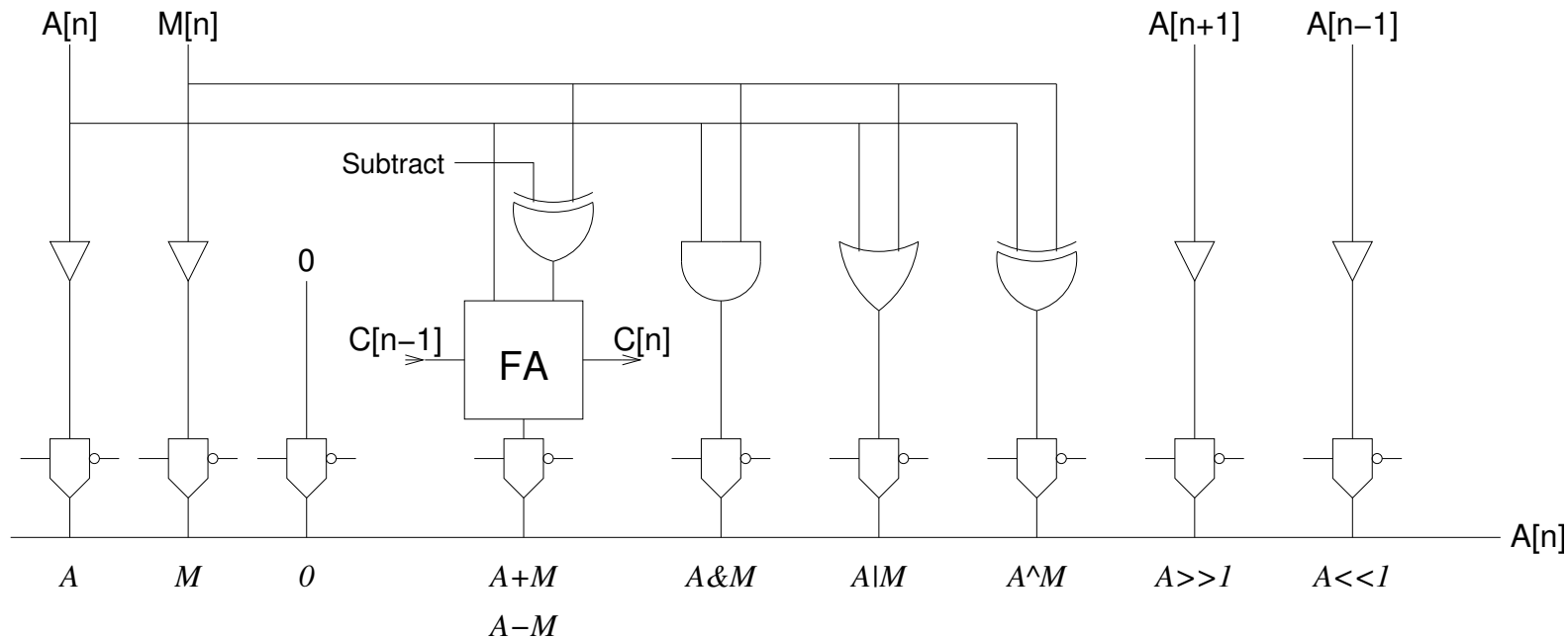
# Bus Distributed Multiplexing

Implementation of bitslice ALU:<sup>5</sup>




- Separate circuit for each function
- Connected via distributed multiplexor

<sup>5</sup>Note that transmission gates have no drive capability in themselves. Here a good drive is ensured by providing buffers.



# Bus Distributed Multiplexing

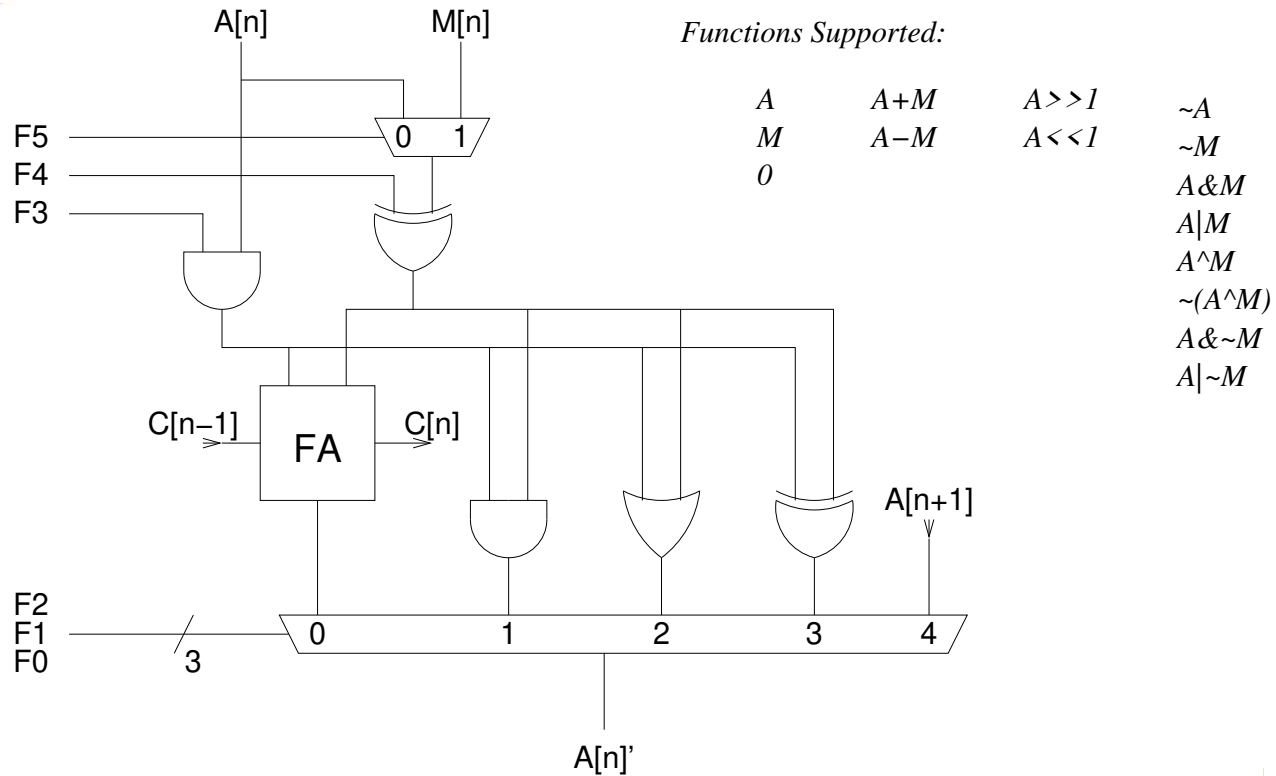


- Single optimized ALU module
- Multiplexing is not distributed
- Multiplexor implementation may use transmission gates

# Pass Transistor Circuits

---

- Tristate Inverter


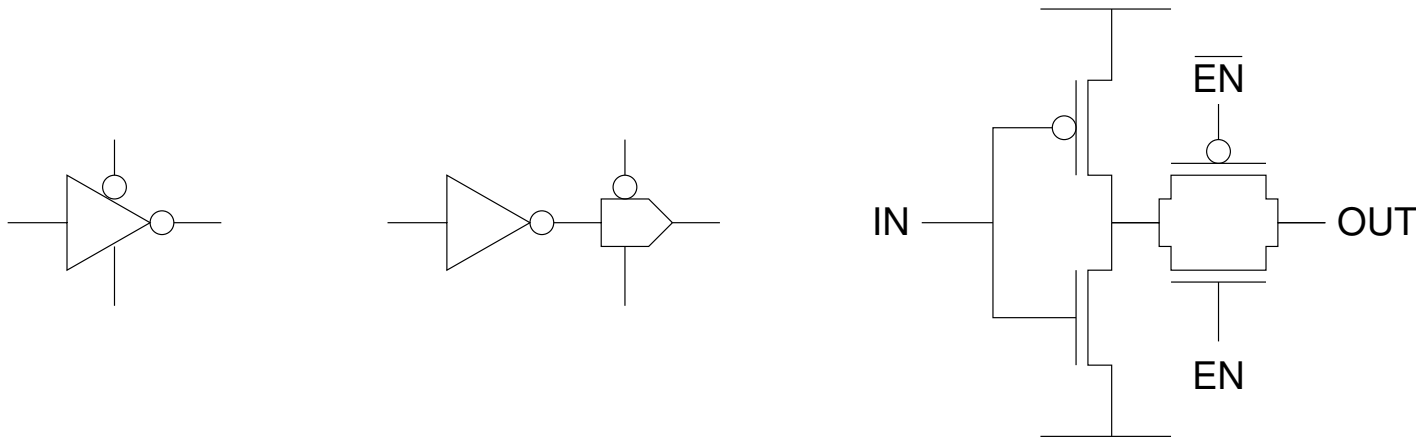


- Any gate may have a tri-state output by combining it with a transmission gate.

# Pass Transistor Circuits

---

- Tristate Inverter

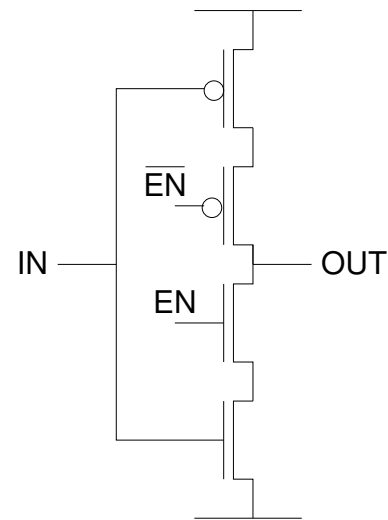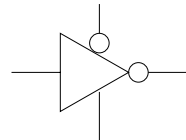


- Alternatively the transmission gate may be incorporated into the gate.
  - - one connection is removed - easier to layout
  - - also easier to simulate!

# Pass Transistor Circuits

---


- Tristate Inverter Layout

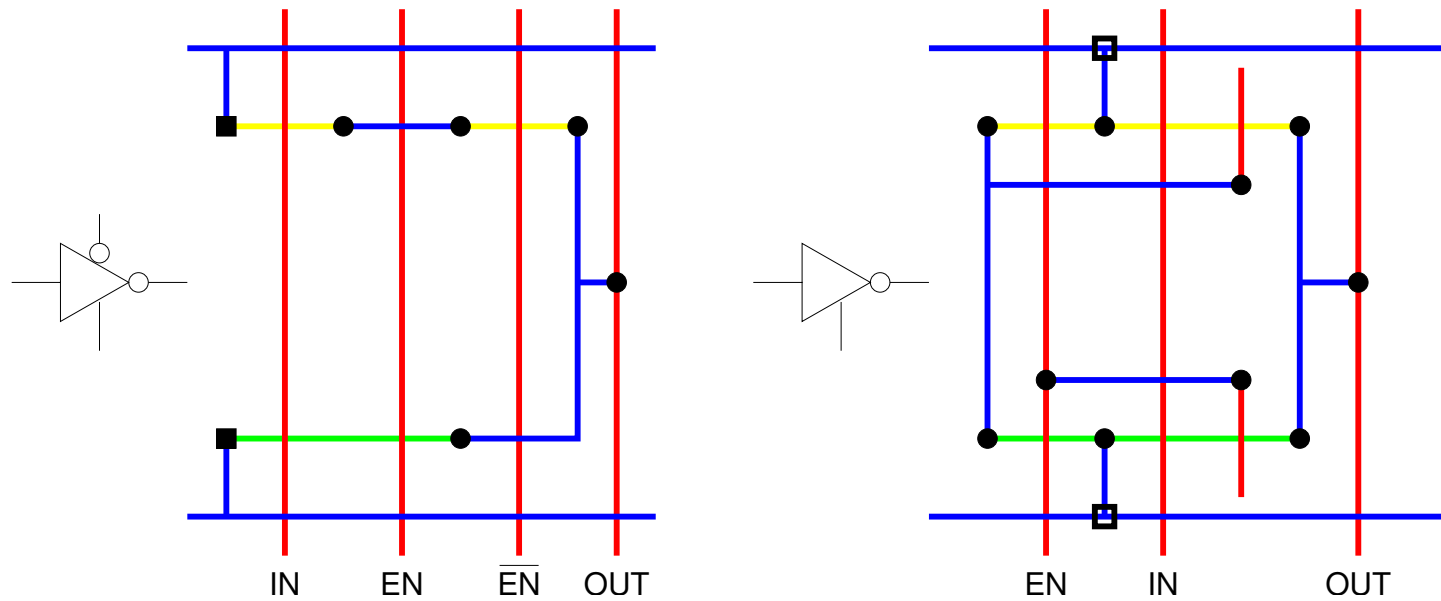

# Pass Transistor Circuits

---

- Tristate Inverter Bus Driver

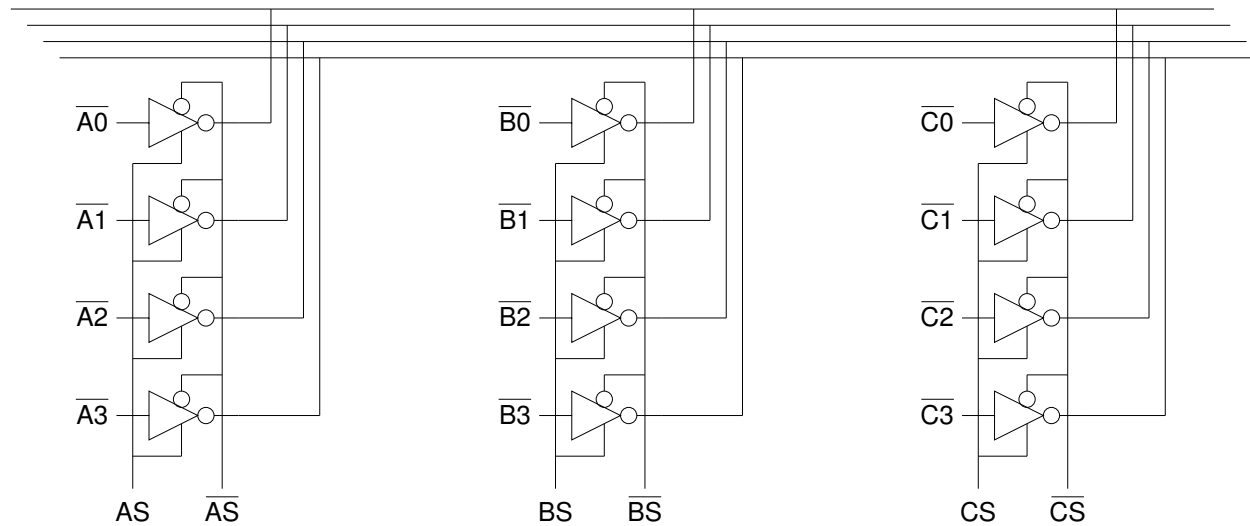

- a tristate inverting buffer is often used to drive high capacitance bus signals
- transistors may be sized as required