

 
 
 
 
 
 


Latch


 


Master Slave D-Type Flip-Flop

 

*multiplexor based latches and flip-flops include distinctive polysilicon crossover

Edge Triggered D-Type Flip-Flop

  

Euler path analysis is applied creatively to these multi-gate cells – gates are often linked via the common gnd/pwr node
Final layouts will be more complex where clock buffers, reset circuitry and metal 2 i/o are included