#### Overview of Technologies

## Components for Logic


Diode

Bipolar Transistors






#### MOS Transistors

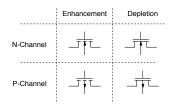




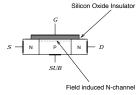


2001

#### Overview of Technologies


RTL Inverter and NOR gate

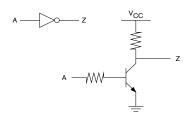

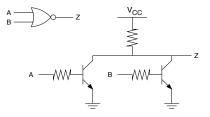
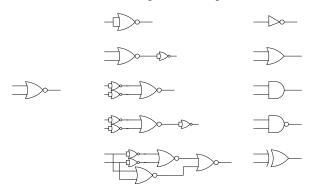
#### Overview of Technologies

All functions can be realized with a single NOR base gate.<sup>1</sup>





<sup>&</sup>lt;sup>1</sup>NAND gates could be used instead.

2003

#### Overview of Technologies

### Other Bipolar Technologies

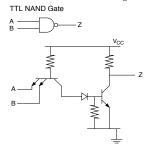

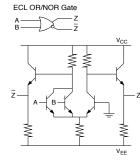


- TTL gives faster switching than RTL at the expense of greater complexity<sup>2</sup>. The characteristic multi-emitter transistor reduces the overall component count.
- ECL is a very high speed, high power, non-saturating technology.

<sup>&</sup>lt;sup>2</sup>Most TTL families are more complex than the basic version shown here

### Overview of Technologies

#### NMOS - a VLSI technology.

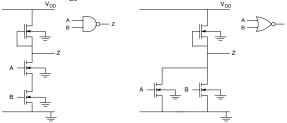


- Circuit function determined by series/parallel combination of devices.
- Depletion transistor acts as non-linear load resistor.
  Resistance increases as the enhancement device turns on, thus reducing power consumption.
- The low output voltage is determined by the size ratio of the devices.

2005

#### Overview of Technologies

#### CMOS logic


CMOS - state of the art VLSI.

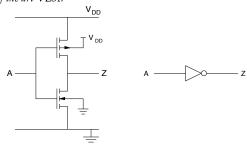

- An active PMOS device complements the NMOS device giving:
  - rail to rail output swing.
  - negligible static power consumption.

#### Digital CMOS Circuits
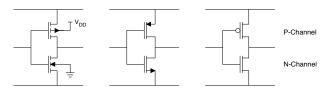
### Alternative representations for CMOS transistors




Various shorthands are used for simplifying CMOS circuit diagrams.

- In general substrate connections are not drawn where they connect to Vdd (PMOS) and Gnd (NMOS).
- All CMOS devices are enhancement mode.
- Transistors act as simple digitally controlled switches.

2007

## Digital CMOS Circuits


#### Static CMOS complementary gates

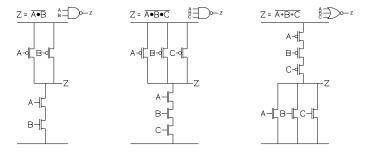

• For any set of inputs there will exist either a path to Vdd or a path to Gnd.

## Digital CMOS Circuits

## Compound Gates

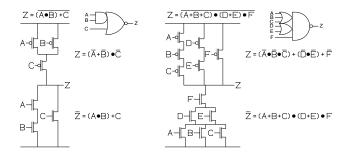

- All compound gates are inverting.
- $\bullet$  Realisable functions are arbitrary AND/OR expressions with inverted output.

2009

## Digital CMOS Circuits

# Compound Gate Example

