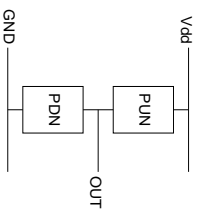


## Static CMOS Complementary Gates



- **Static**  
After the appropriate propagation delay the output becomes valid and remains valid.<sup>1</sup>

- **Complementary**

For any set of inputs there will exist either a path to Vdd or a path to GND.


Where this condition is not met we have either a high impedance output or a conflict in which the strongest path succeeds. Static CMOS **Non-complementary** gates make use of these possibilities.

<sup>1</sup>cf. Dynamic logic which uses circuit capacitance to store state for a short time.

7001

## Pass Transistor Circuits

- Pass Transistor

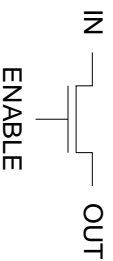

- Provides very compact circuits.
- Good transmission of logic '0'.
- Poor transmission of logic '1'.
- slow rise time
- degradation of logic value

The pass transistor is used in many dynamic CMOS circuits<sup>2</sup>.


<sup>2</sup>where pull-up is performed by an alternative method

7002
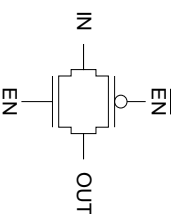
## Pass Transistor Circuits

- Transmission Gate

- For static circuits we would normally use a CMOS transmission gates:




- balanced *n* and *p* pass transistors
- faster pull-up
- slower pull-down

7003

## Pass Transistor Circuits

- Transmission Gate Layout

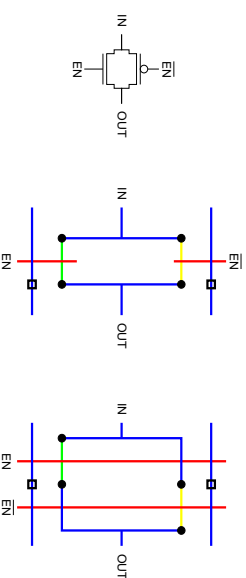


- note that these circuits are not fully complementary<sup>3</sup> hence they do not immediately lend themselves to a *line of diffusion* implementation.

<sup>3</sup>since there are sets of inputs for which the output is neither pulled low nor high

7004

## Pass Transistor Circuits

- Transmission Gate Multiplexor

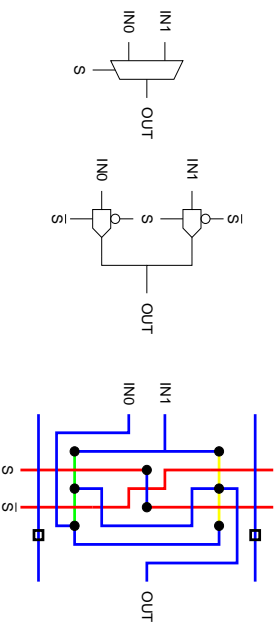


- very few transistors 4 (+2 for inverter)
- difficult layout may offset this advantage
- - prime candidate for 2 level metal

7005

## Pass Transistor Circuits

- Bus Wiring

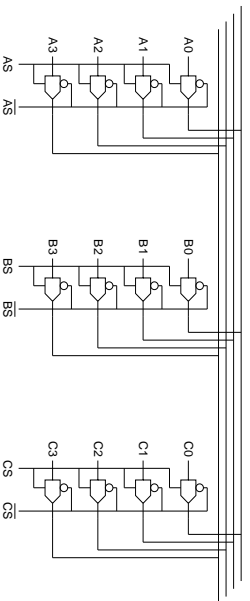


- distributed multiplexing<sup>4</sup>
- only one inverter required per bank of transmission gates
- greatly simplifies global wiring

<sup>4</sup>internal chip bus should never be allowed to float high impedance

7006

## Bus Distributed Multiplexing

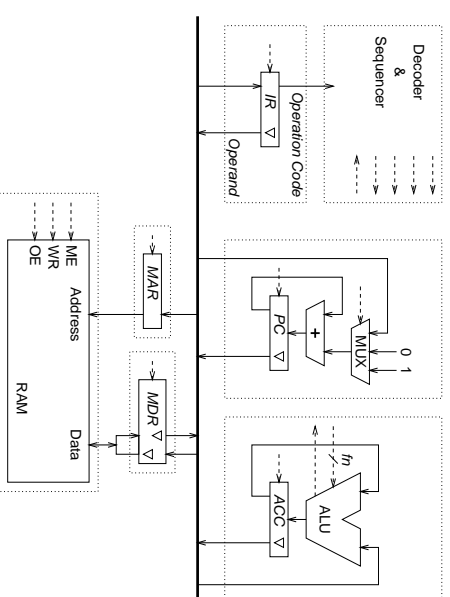


Ideal for signals with many drivers from different modules.

7007

## Bus Distributed Multiplexing
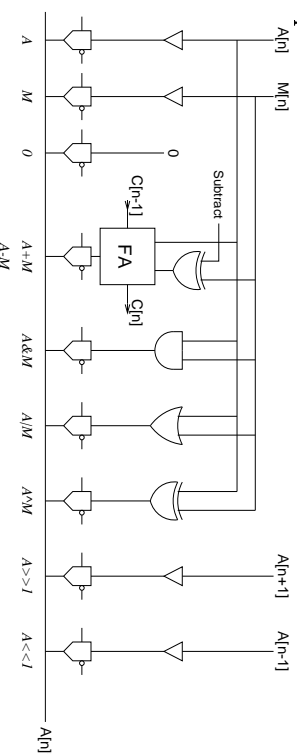
### Implementation of bit-slice ALU:<sup>5</sup>




- Separate circuit for each function
- Connected via distributed multiplexor

<sup>5</sup>Note that transmission gates have no drive capability in themselves. Here a good drive is ensured by providing buffers.

7008

## Bus Distributed Multiplexing

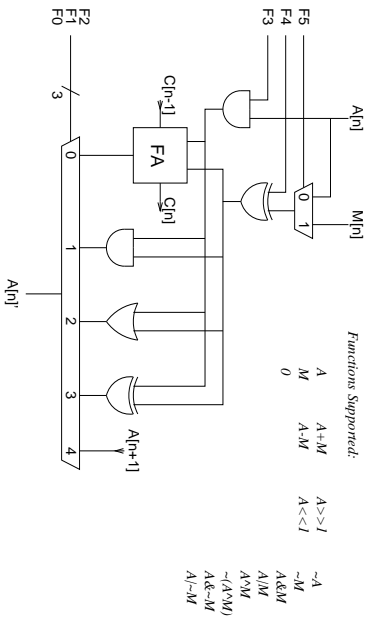


- Single optimized AIU module
- Multiplexing is not distributed
- Multiplexor implementation may use transmission gates

7009

## Pass Transistor Circuits

- Tristate Inverter

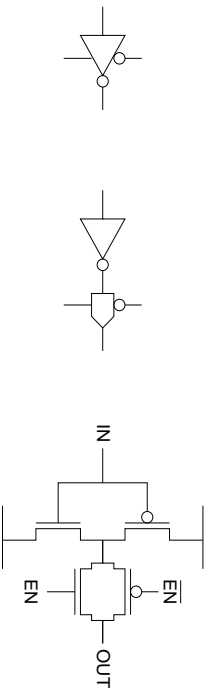


- Any gate may have a tri-state output by combining it with a transmission gate.

7010

## Pass Transistor Circuits

- Tristate Inverter

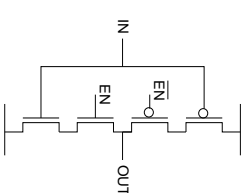


- Alternatively the transmission gate may be incorporated into the gate.  
 - - one connection is removed - easier to layout  
 - - also easier to simulate!

7011

## Pass Transistor Circuits

- Tristate Inverter Layout

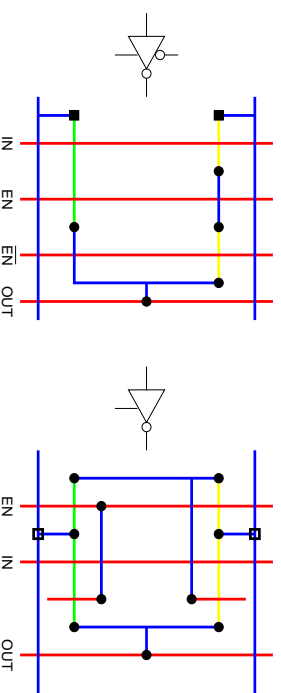


7012

## Pass Transistor Circuits

---

- Tristate Inverter Bus Driver

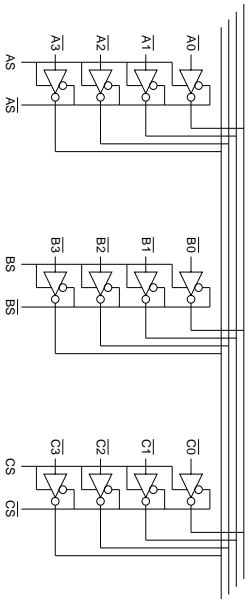

- a tristate inverting buffer is often used to drive high capacitance bus signals
- transistors may be sized as required