
 



1947 Point Contact transistor

 


Source: Bell Labs



1961 Fairchild Bipolar RTL RS Flip-Flop

 


Source: Fairchild

 


Moore's Law (1965) Number of transistor has doubled every year and will continue to do so until 1975

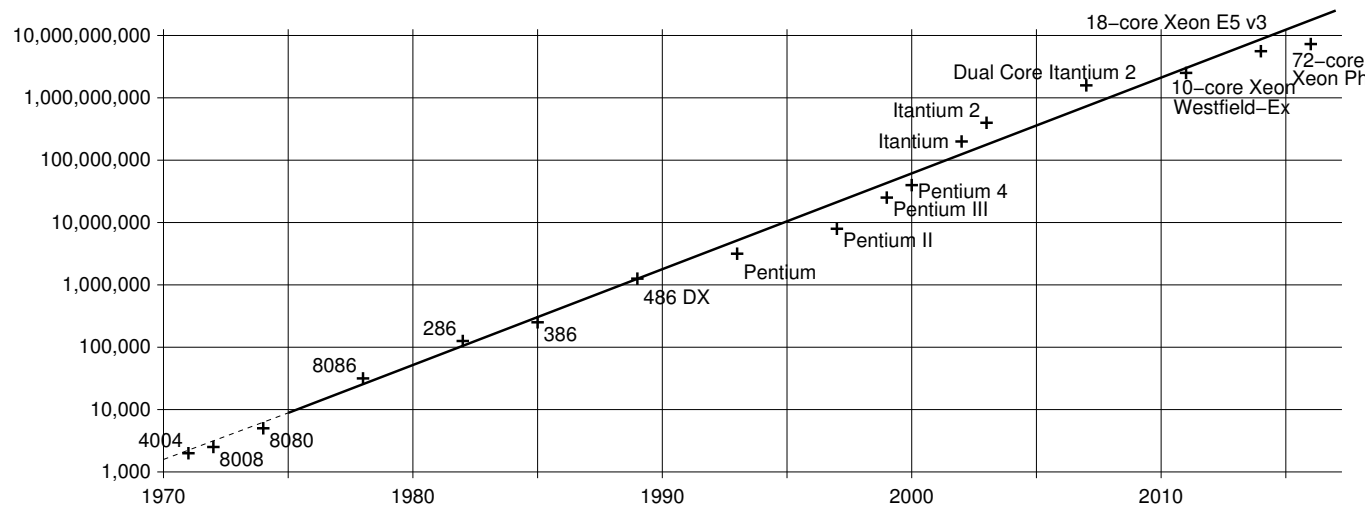Moore's Law (1975) Number of transistors will double every two years




Self-fulfilling Prophecy


RTL NOR Gate

 


TTL NAND Gate

 



ECL OR/NOR Gate

 

NMOS Compound Gate

 

CMOS Compound Gate

  

- Bipolar Transistors with Resistors - MSI/LSI

RTL - NOR

TTL - NAND

ECL - OR/NOR


- MOS Transistors (no resistors) - VLSI

NMOS


CMOS - No static power!

*Both allow construction of NOR, NAND & Compound gate (always inverting)*


Diode

 


NPN Transistor

 


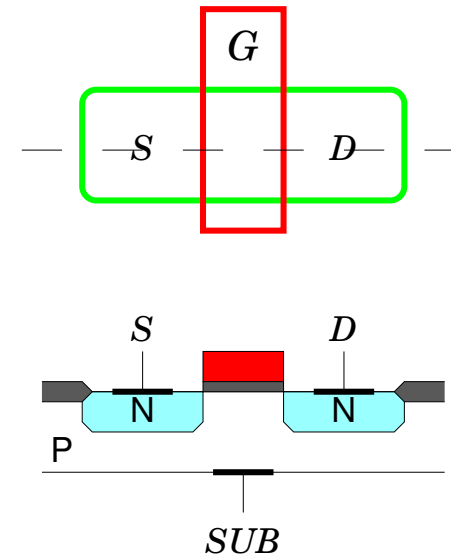
NMOS Enhancement transistor  
NMOS Process




Resistor

 


Capacitors

  


PMOS Enhancement transistor CMOS Process

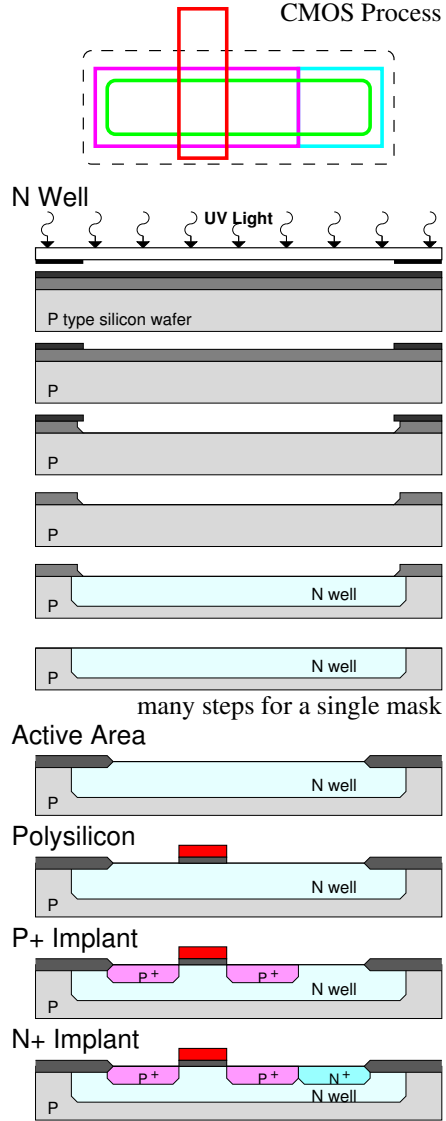


CMOS Inverter Twin Tub CMOS Process

 

 CMOS Inverter N-Well CMOS Process (with explicit N+ implant mask)




 CMOS Inverter N-Well CMOS Process (without explicit N+ implant mask)




Features may be determined by a number of masks  
 e.g. NMOS source drain: ActiveArea AND NOT(NWell OR Poly OR PImplant)

 
Design Rules – width, separation, overlap



Optimised Mask Layout


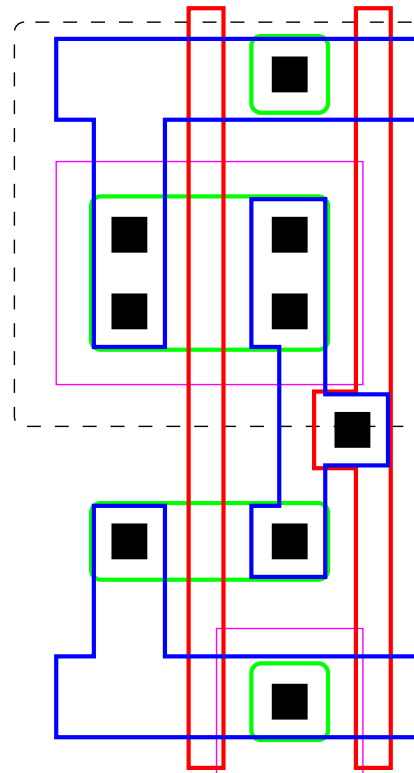


Equivalent Stick Diagram

 

- Metal
- Polysilicon
- N+
- P+
- Contact
- Tap
- Combined contact & tap

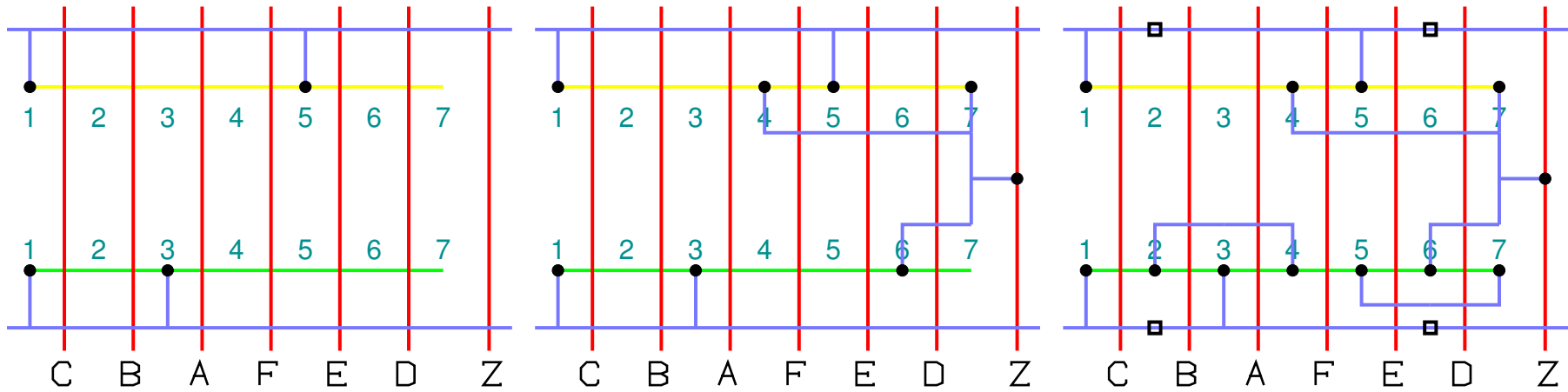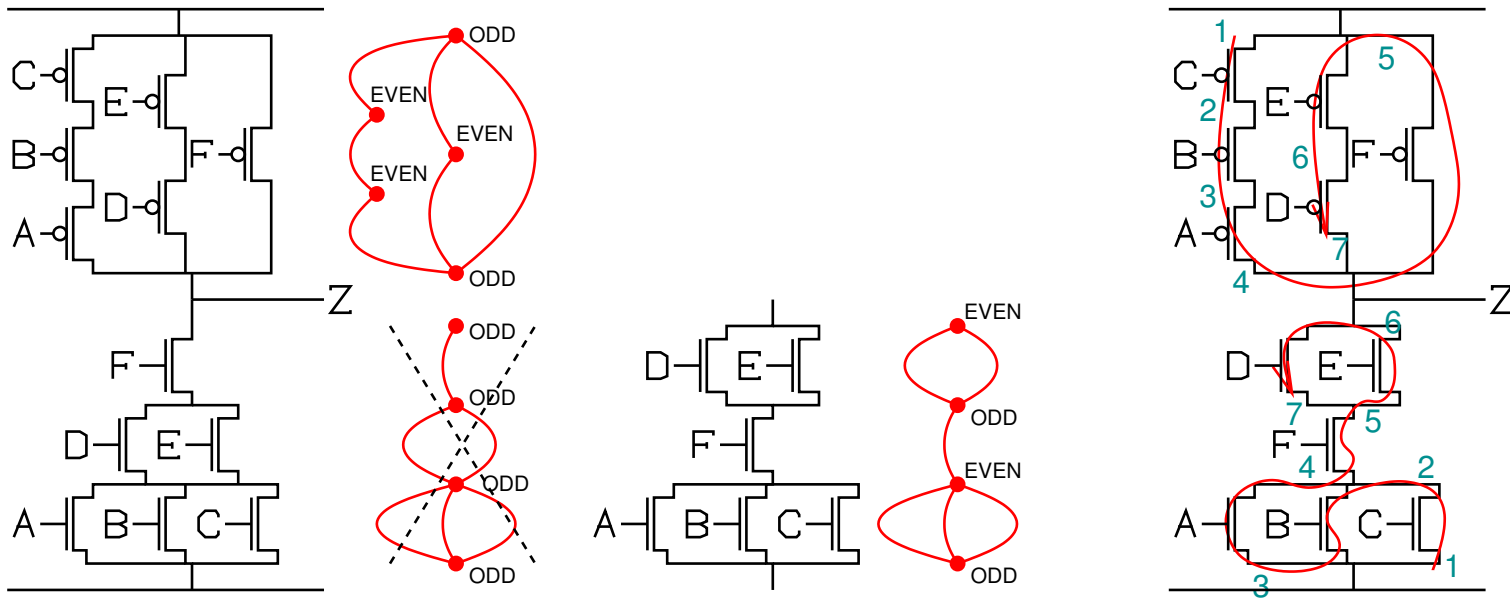
# Investigation of Euler paths leads to more efficient layout\*




\*not all gates will support a common Euler path for both PMOS and NMOS

**1 METAL LAYER**



**LAYOUT**

 





**ABSTRACT**

 






**ROUTING**

  


**2 METAL LAYERS**

    



**3 METAL LAYERS**

     



### Pass Transistor

 

### CMOS Transmission Gate

  

### Transmission Gate Multiplexor

  


\*note distinctive polysilicon crossover


### Tri-state gates are used for Multiplexing

#### Distributed Multiplexing


using transmission gates

 




using tri-state inverters

 



using tri-state buffers

 


### Tri-state Inverter

   

### Tri-state Buffer

  





#### Bi-directional I/O

 





\*this is another form of multiplexing



Latch

   
 


Master Slave D-Type Flip-Flop

    


\*multiplexor based latches and flip-flops include distinctive polysilicon crossover

Edge Triggered D-Type Flip-Flop

  


Euler path analysis is applied creatively to these multi-gate cells – gates are often linked via the common gnd/pwr node  
Final layouts will be more complex where clock buffers, reset circuitry and metal 2 i/o are included

## PLA and ROM

 




AND Plane

OR Plane

 


ROM is PLA with  
fixed AND (decoder) plane  
programmable OR (data) plane

## SRAM

   

Cells are designed to butt together in two dimensions leading to efficient layout

 PLA layout efficiency will depend on the actual function implemented (e.g. number of common product terms)



All design styles need full custom designers

A large ASIC (especially SoC) may mix Semi-Custom and Full Custom