

# Digital CMOS Design

---

## Taps

For simple functionality we require only one tap per N well and a single tap for the whole wafer substrate.<sup>1</sup> Unfortunately CMOS circuits can fail due to *Latch-up*, a condition in which the whole chip acts as a thyristor (PNPN) device in order to short Vdd to Vss.




The following (process independent) guidelines should be considered when deciding on a cell layout.

- Every well must have an appropriate tap.
- Every tap must be connected to a supply pad via unbroken metal.
- Taps should be placed as close to source connections as possible.
- Empirical rule: one tap for every 5-10 transistors.
- Layout N devices packed towards Vss and P devices packed towards Vdd.

---

<sup>1</sup>Assuming an N well process.

## Latch-up

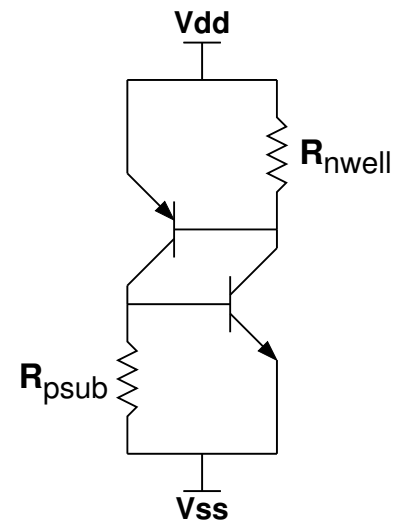  


# Digital CMOS Design

---


## Choosing a Layout

Frequently there are several possible Euler paths for the same gate. Given that all cells must have taps, the position of the taps may effect your choice.


$$Z = \overline{(A \bullet B)} + C$$

 

(1)

 

(2)

 


(3)

# Digital CMOS Design

---
 
## Choosing a Layout

Given an identical Euler path we still have choices such as tap location.



# Digital CMOS Design

---

## Choosing a Layout

There is no best layout for any cell.

There are always other considerations:

- Performance:
  - Minimum source-drain capacitance.
  - Ratio of P and N device sizes.
  - Ratio of series device sizes.
- Co-existence:
  - Geometry of other cells.
  - Routing Considerations.