
 


Latches and Flip-Flops

- CMOS transmission gate latch


 


A simple transparent latch can be build around a transmission gate multiplexor

- transparent when load is high
- latched when load is low
- two inverters are required since the transmission gate cannot drive itself

Latches and Flip-Flops



- Transmission gate latch layout

  

– a compact layout is possible using 2 layer metal

Latches and Flip-Flops

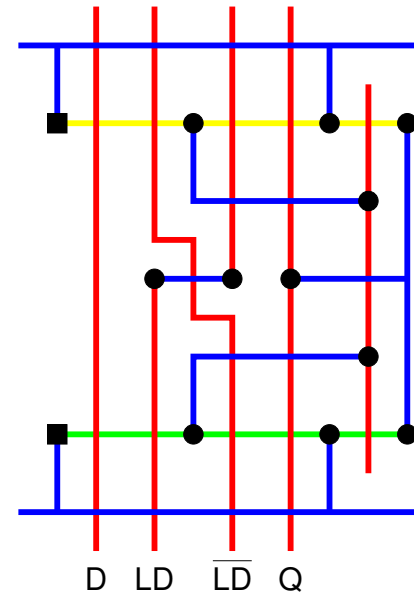 
- A simpler layout may be achieved using tristate inverters.



- this design requires two additional transistors but may well be more compact.

Latches and Flip-Flops

 
- For use in simple synchronous circuits we use a pair of latches in a master slave configuration.




- this avoids the race condition in which a transparent latch drives a second transparent latch operating on the same clock phase.
- the circuit behaves as a rising edge triggered D type flip-flop.

Latches and Flip-Flops

- Transmission gate implementation

 


- Tristate inverter implementation

 


Latches and Flip-Flops

- Alternative configuration


 


– Implementation

 

Latches and Flip-Flops


- Layout of master slave D type.

  

– very compact using alternative configuration.

Latches and Flip-Flops

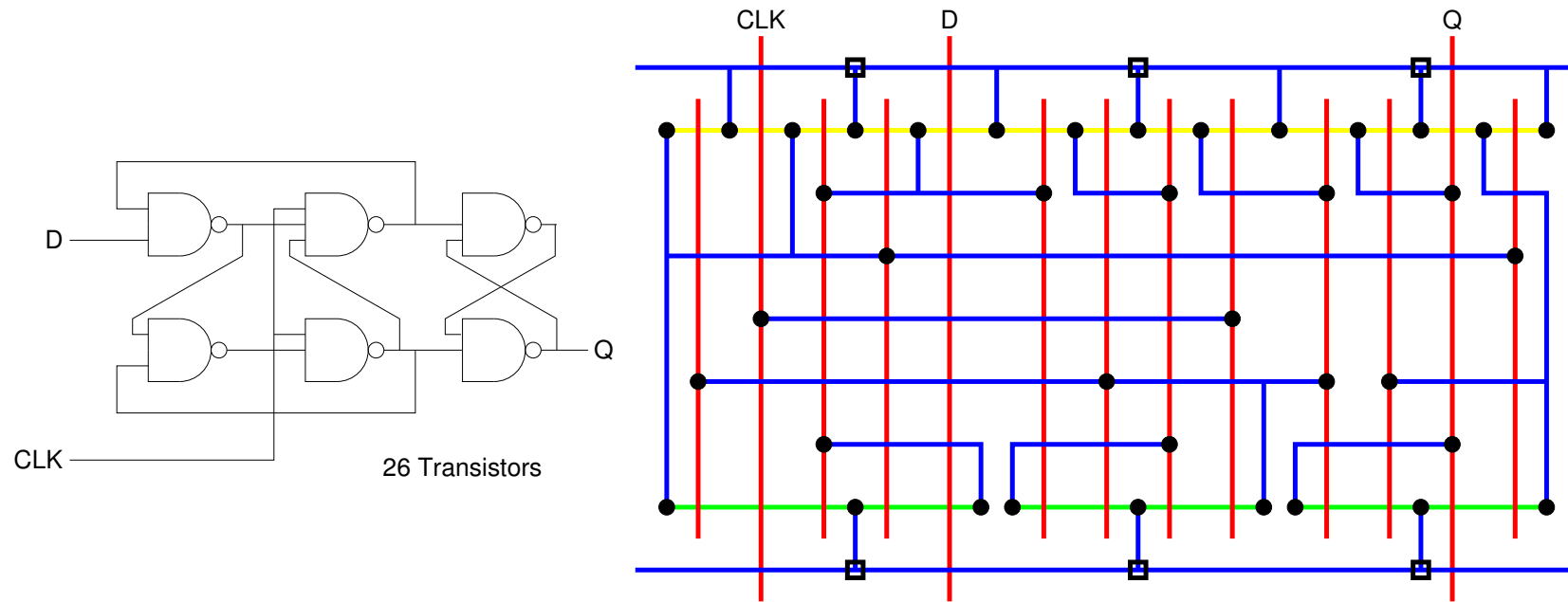
- For the same functionality we could use an edge triggered D type:



- a few more transistors
- more complex wiring
- simpler clock distribution

Register File

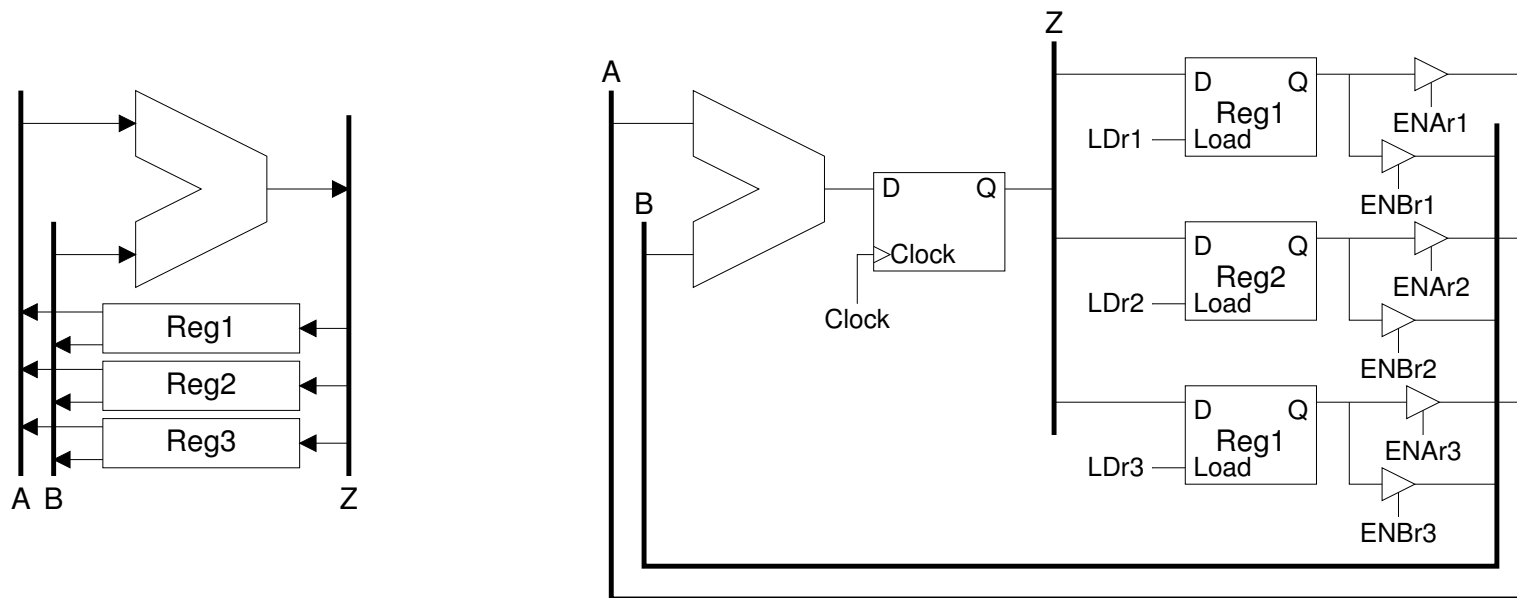Where we have large amounts of storage the use of individual latches can lead to space saving.



- Load signals must be glitch free with tightly controlled timing.
- Edge Triggered D-type prevents a race condition ($Reg1 \leftarrow Reg1 + Reg2$).