

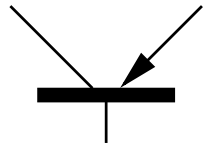
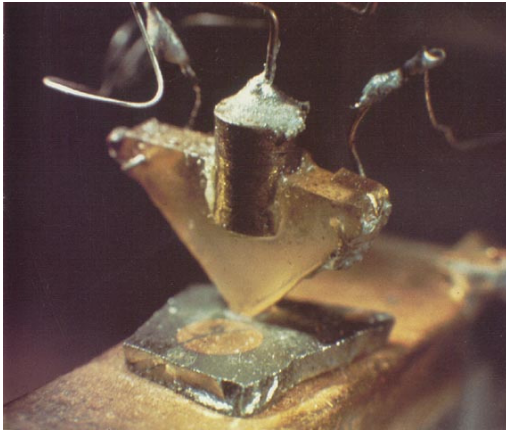


1947 Point Contact transistor

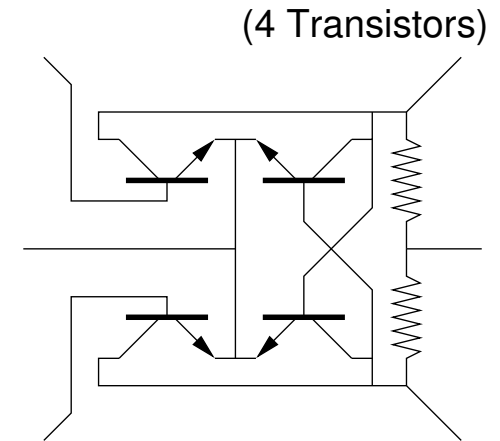


1961 Fairchild Bipolar RTL RS Flip-Flop

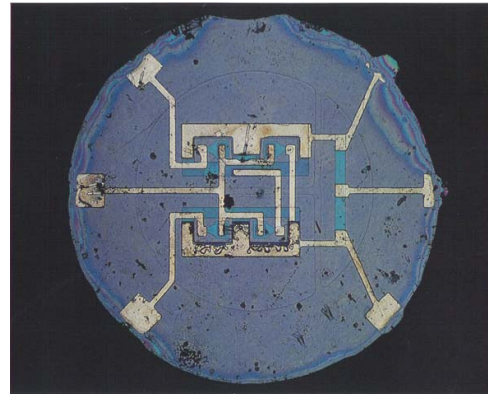

1965 Moore's Law (Mk I) Number of transistor has doubled every year and will continue to do so until 1975


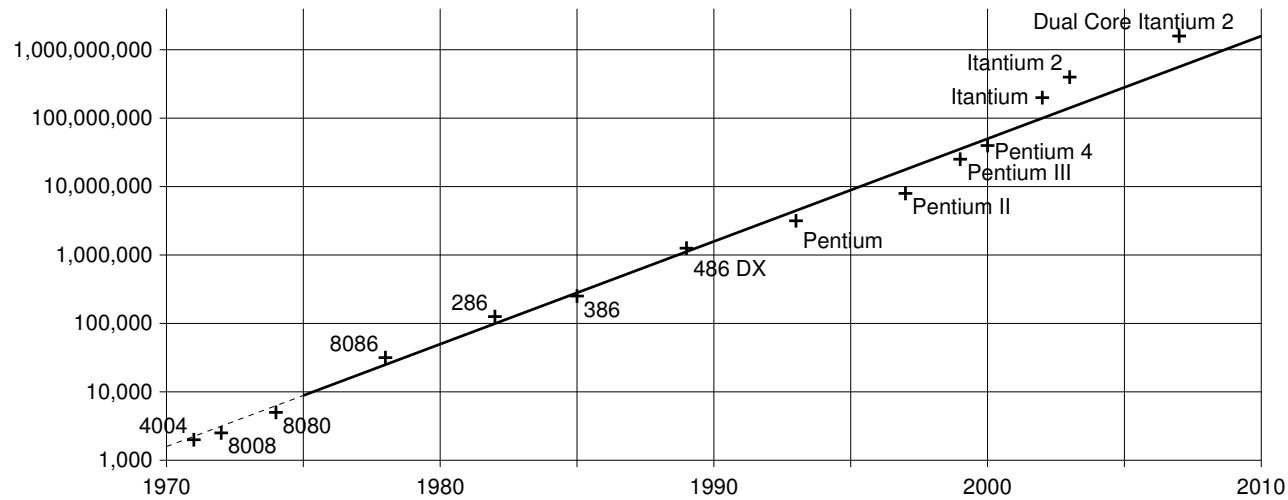
1975 Moore's Law (Mk II) Number of transistors will double every two years





Self-fulfilling Prophecy

1000


RTL NOR Gate

  


TTL NAND Gate

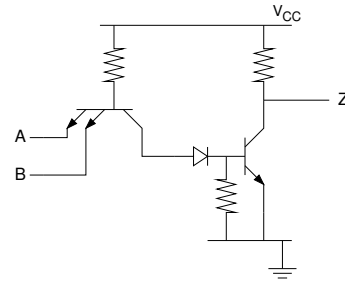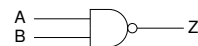



ECL OR/NOR Gate

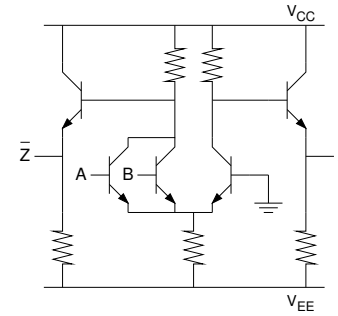

NMOS Compound Gate

 

CMOS Compound Gate

 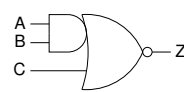

- Bipolar Transistors with Resistors - MSI/LSI

RTL - NOR

TTL - NAND

ECS - OR/NOR


- MOS Transistors (no resistors) - VLSI

NMOS


CMOS - No static power!

*Both allow construction of NOR, NAND & Compound gate (always inverting)*


Diode

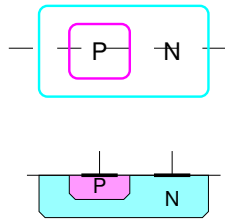


NPN Transistor

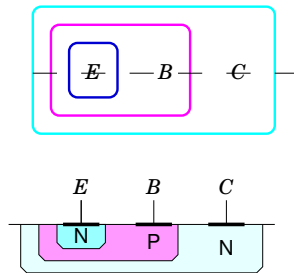

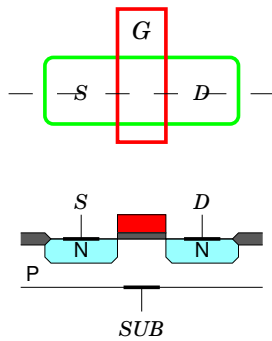NMOS Enhancement transistor  
NMOS Process




CMOS Inverter

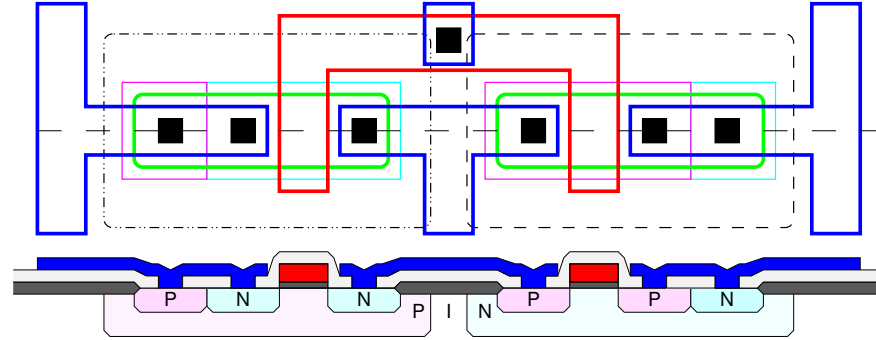

Twin Tub CMOS Process


CMOS Inverter

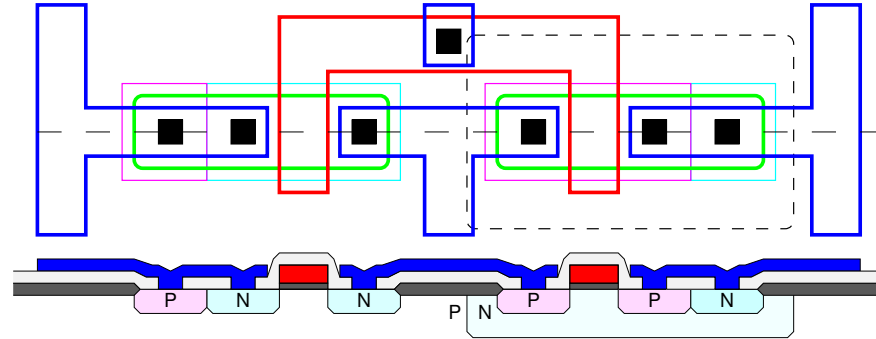N-Well CMOS Process (with explicit N+ implant mask)




CMOS Inverter

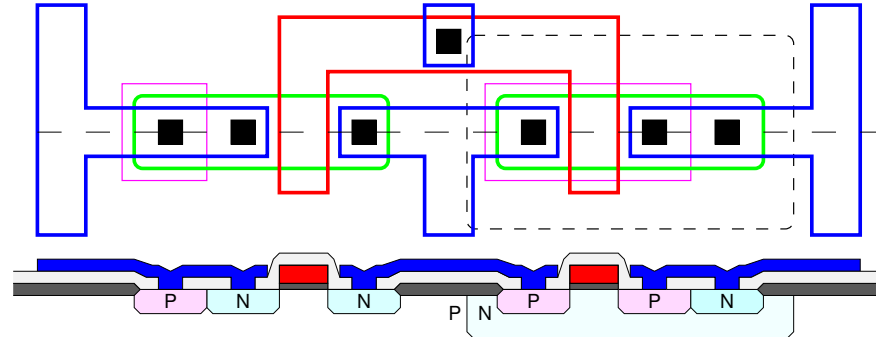N-Well CMOS Process (without explicit N+ implant mask)




Features may be determined by a number of masks  
 e.g. NMOS source drain: ActiveArea AND NOT(NWell OR Poly OR PImplant)


Processing

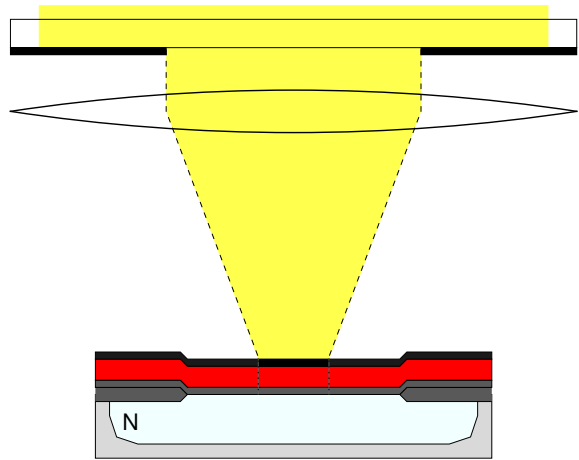


Optimised Mask Layout

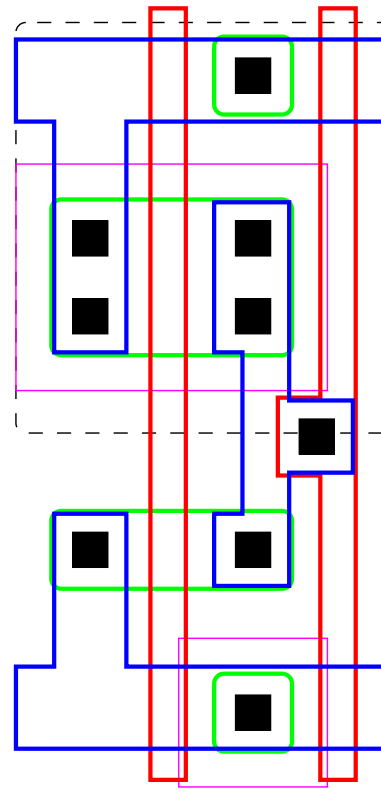

Equivalent Stick Diagram


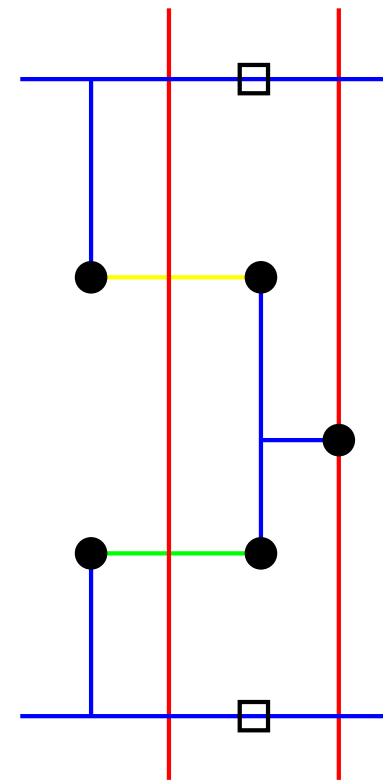


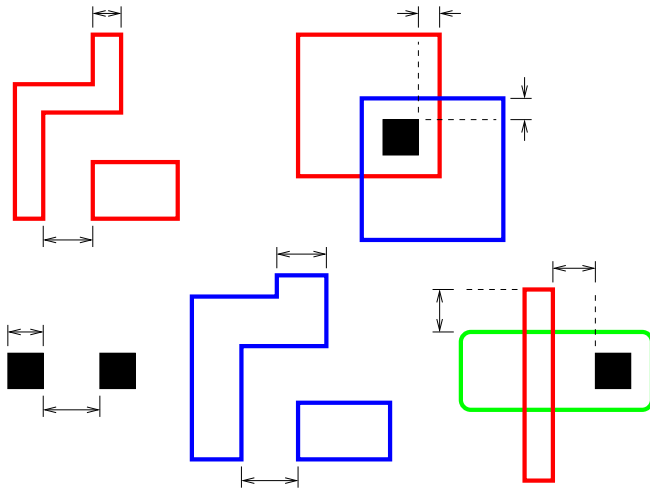Design Rules – width, separation, overlap



- Metal
- Polysilicon
- N+
- P+
- Contact
- Tap
- Combined contact & tap

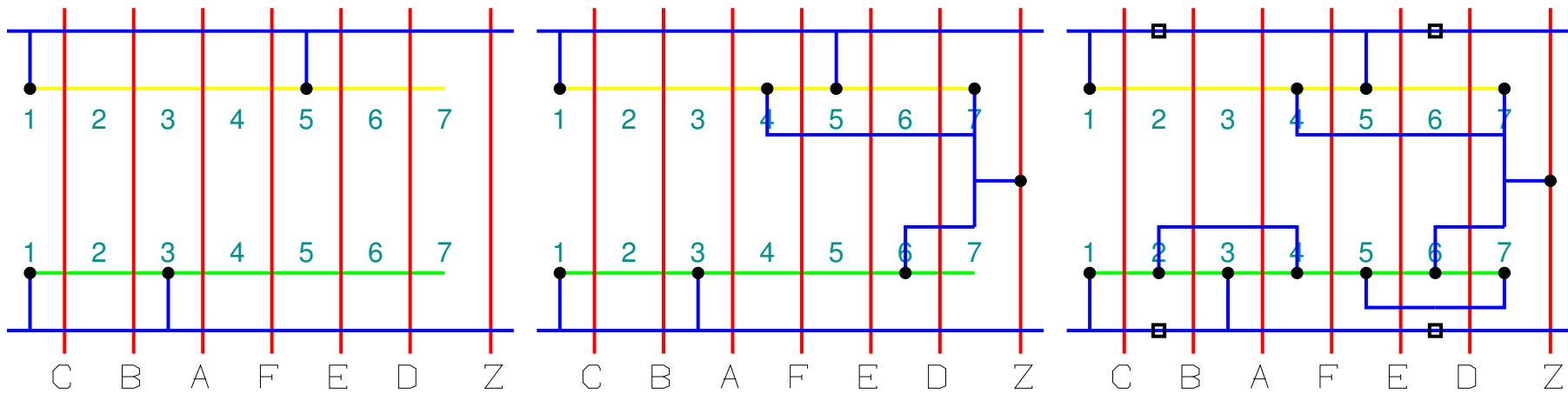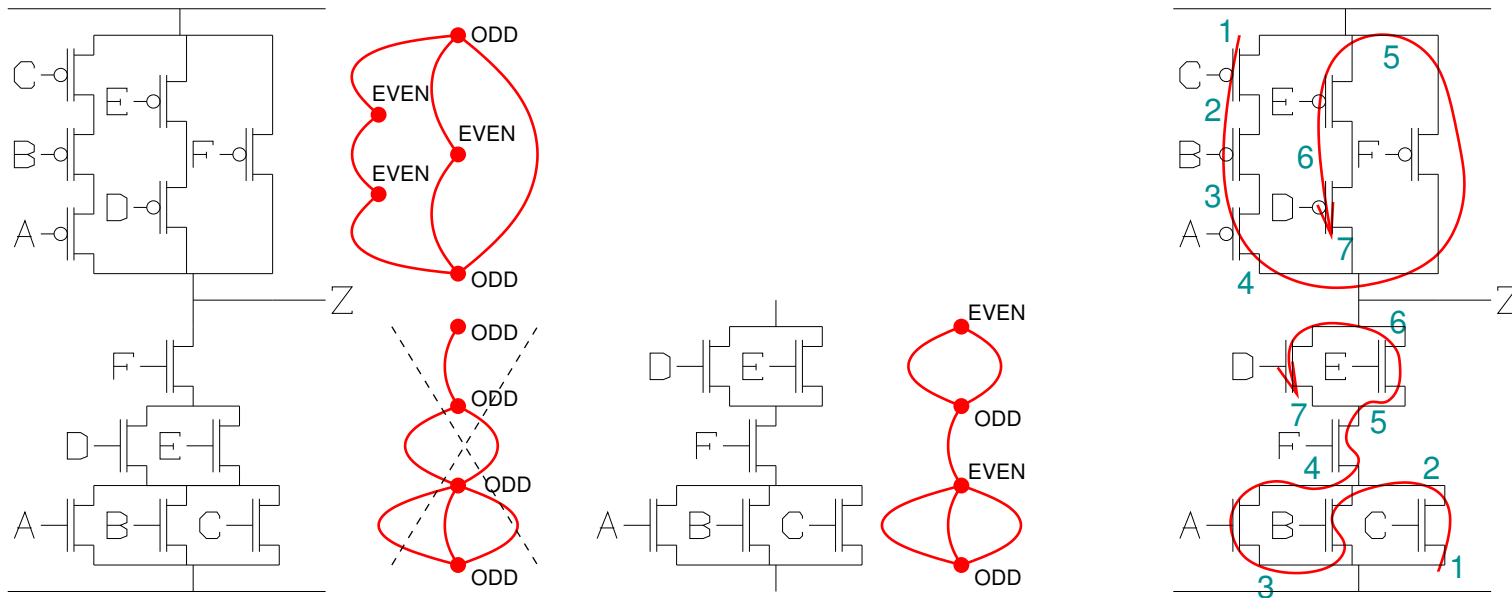
# Investigation of Euler paths leads to more efficient layout\*




\*not all gates will support a common Euler path for both PMOS and NMOS

**1 METAL LAYER**



**LAYOUT**

 

**ABSTRACT**

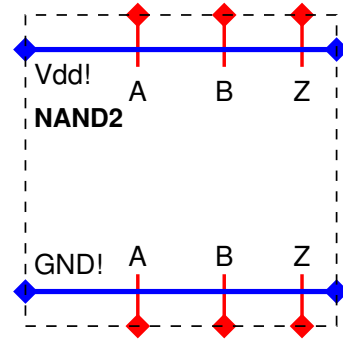


**ROUTING**

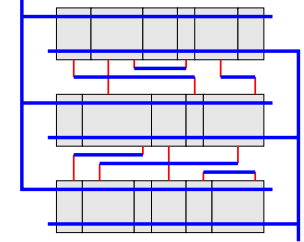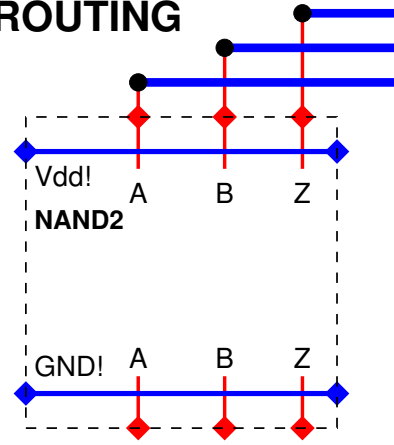


**2 METAL LAYERS**



**LAYOUT**

 

**ABSTRACT**

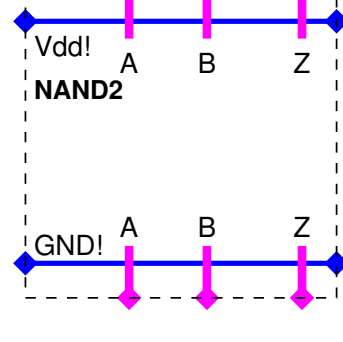


**ROUTING**

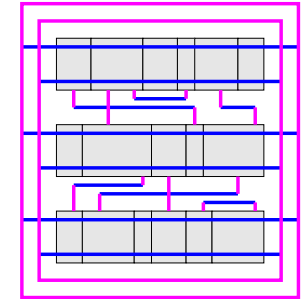 


**3 METAL LAYERS**




**LAYOUT**

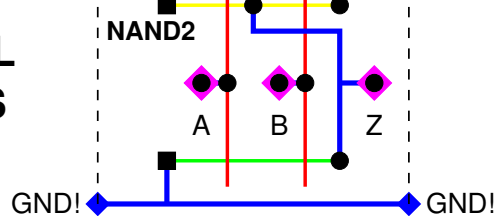


**ABSTRACT**

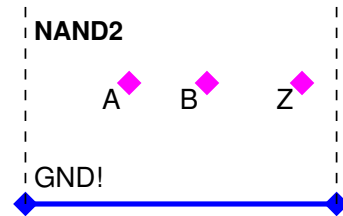



**ROUTING**

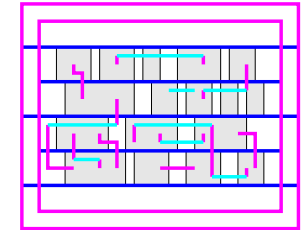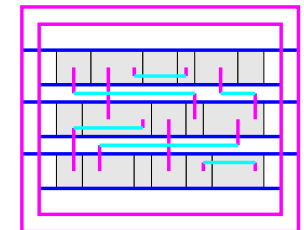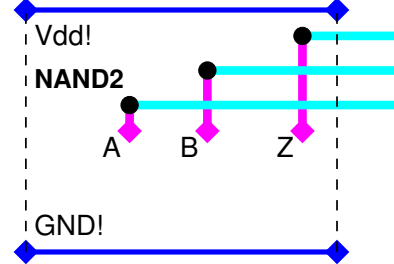



### Pass Transistor

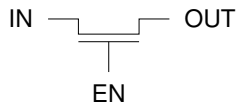

### CMOS Transmission Gate

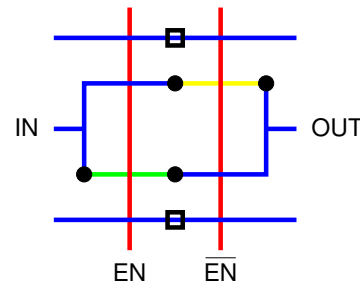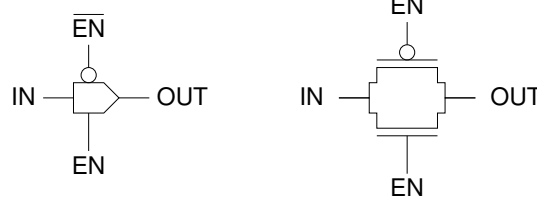

### Transmission Gate Multiplexor

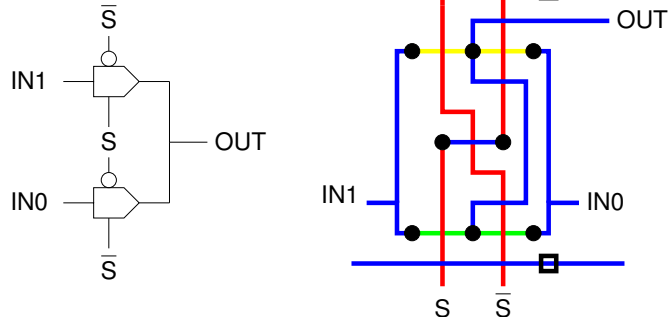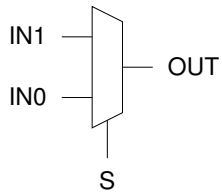


\*note distinctive polysilicon crossover


Tri-state gates are used for Multiplexing

#### Distributed Multiplexing


using transmission gates

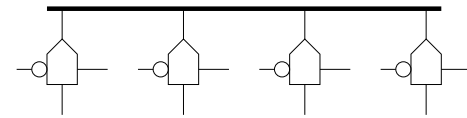




using tri-state inverters

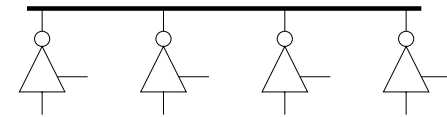



using tri-state buffers

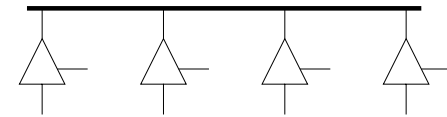


### Tri-state Inverter

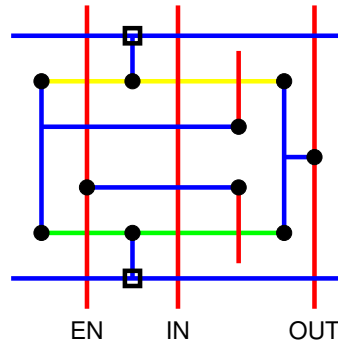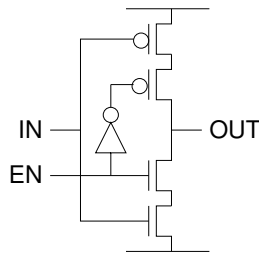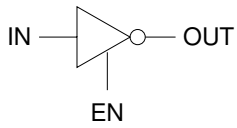

### Tri-state Buffer



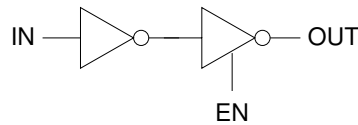
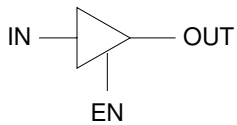


#### Bi-directional I/O




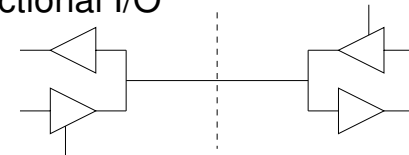


\*this is another form of multiplexing

### Latch

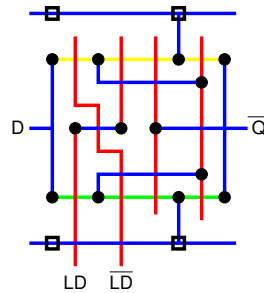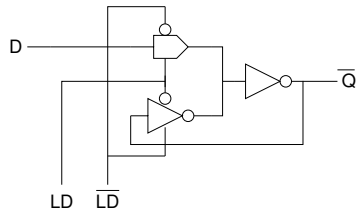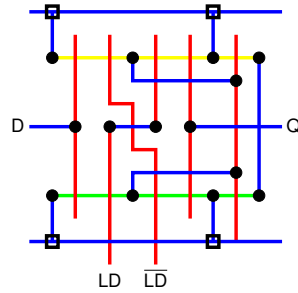
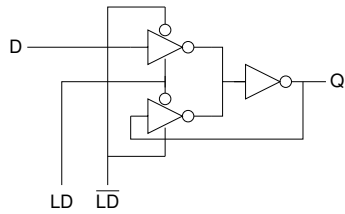


### Master Slave D-Type Flip-Flop

  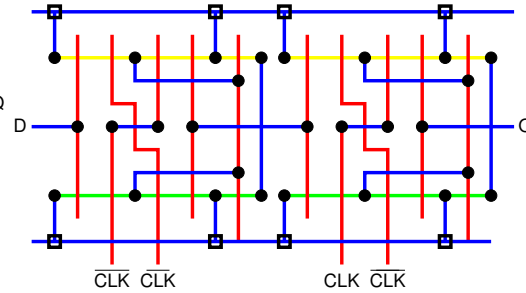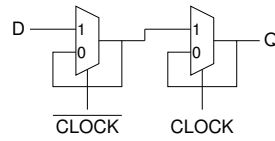

\*multiplexor based latches and flip-flops include distinctive polysilicon crossover


### Edge Triggered D-Type Flip-Flop

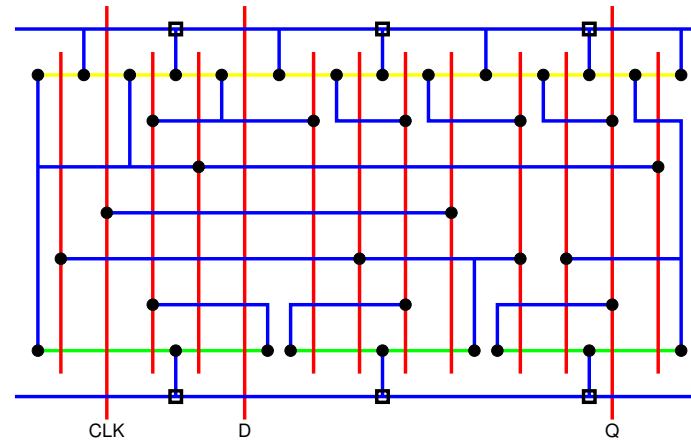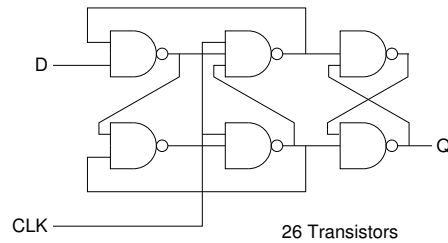

Euler path analysis is applied creatively to these multi-gate cells – gates are often linked via the common gnd/pwr node  
Final layouts will be more complex where clock buffers, reset circuitry and metal 2 i/o are included




## PLA and ROM

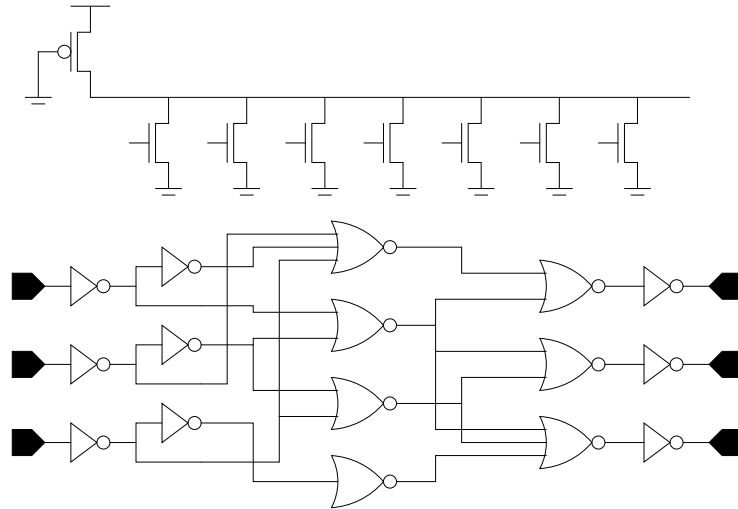




AND Plane

OR Plane

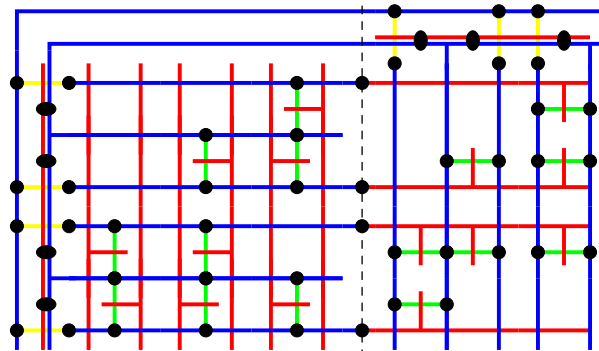


ROM is PLA with  
fixed AND (decoder) plane  
programmable OR (data) plane

## SRAM

 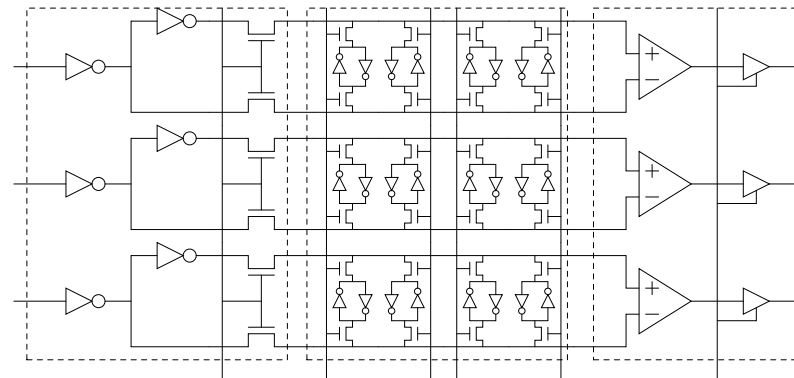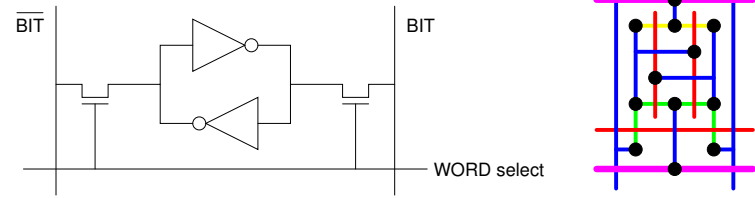

Cells are designed to butt together in two dimensions leading to efficient layout

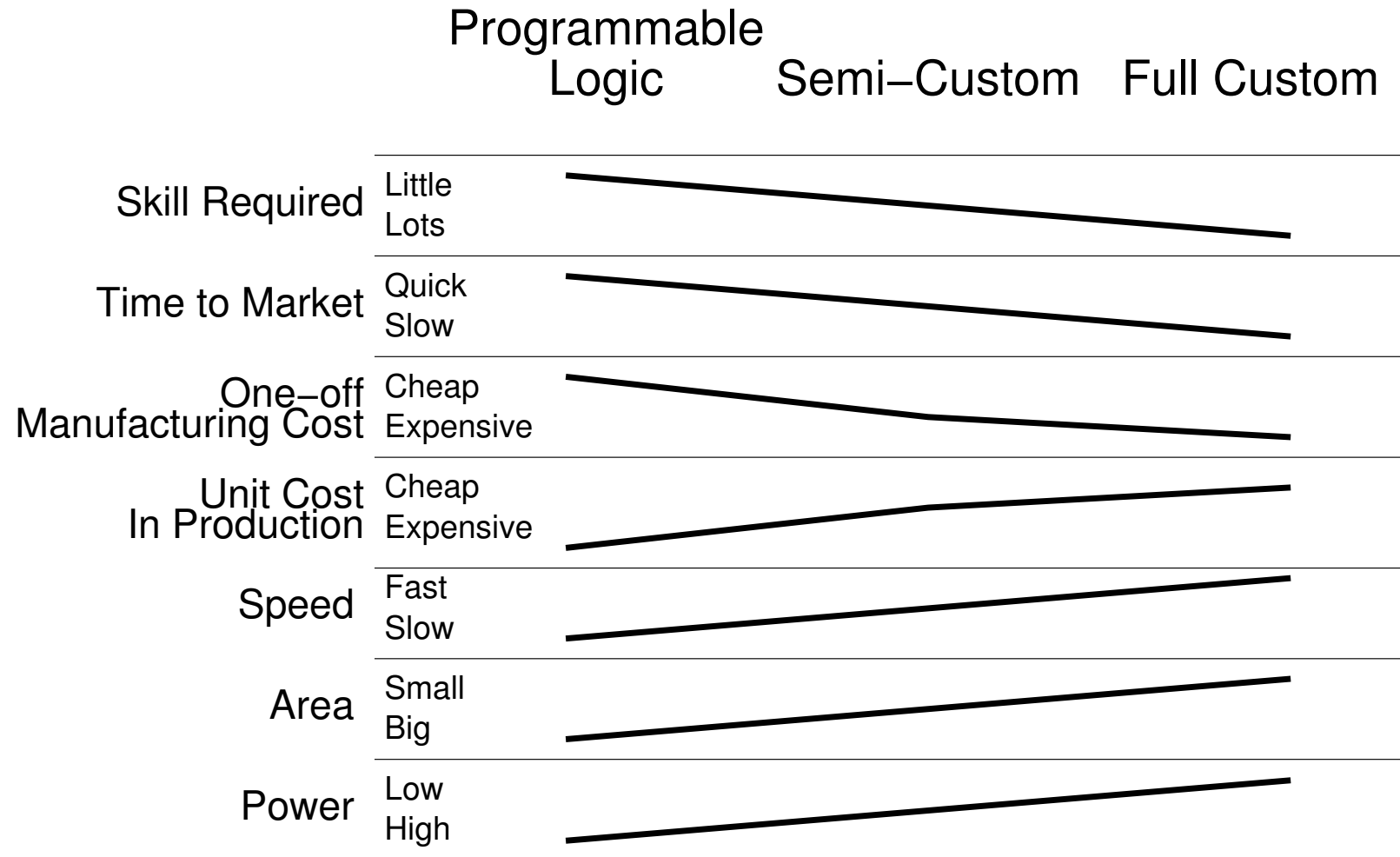PLA layout efficiency will depend on the actual function implemented (e.g. number of common product terms)



All design styles need full custom designers

A large ASIC (especially SoC) may mix Semi-Custom and Full Custom