
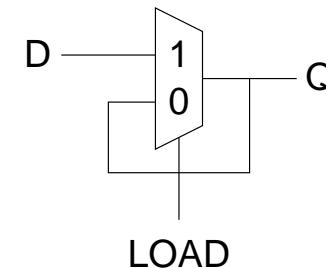


# Latches and Flip-Flops

---

- CMOS transmission gate latch

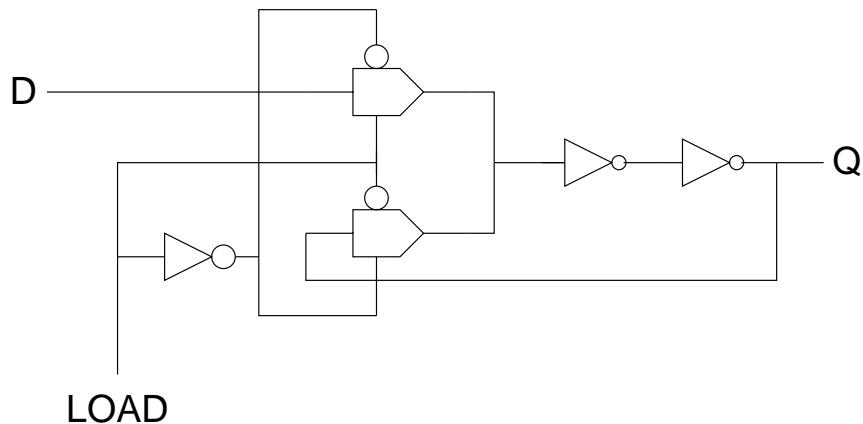



A simple transparent latch can be build around a transmission gate multiplexor

- transparent when load is high
- latched when load is low
- two inverters are required since the transmission gate cannot drive itself

# Latches and Flip-Flops

---

- Transmission gate latch layout

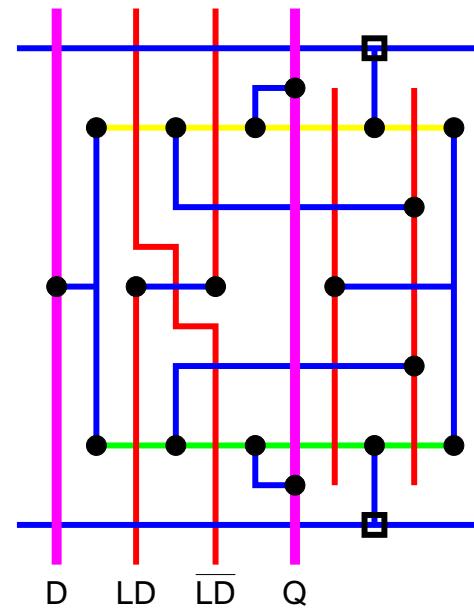
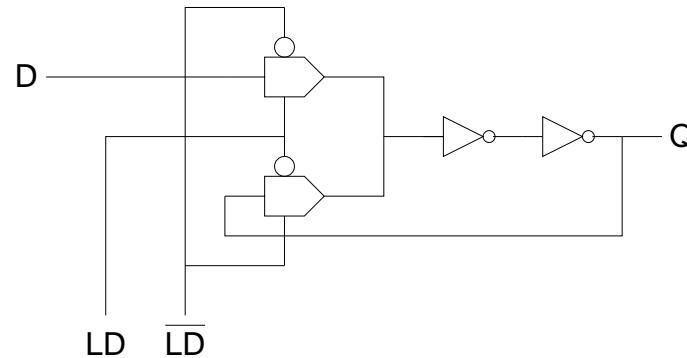


- a compact layout is possible using 2 layer metal
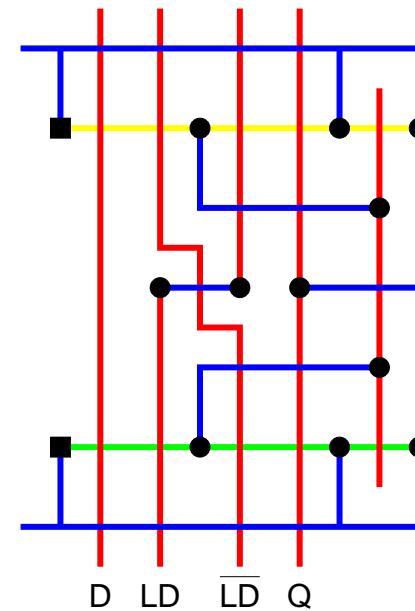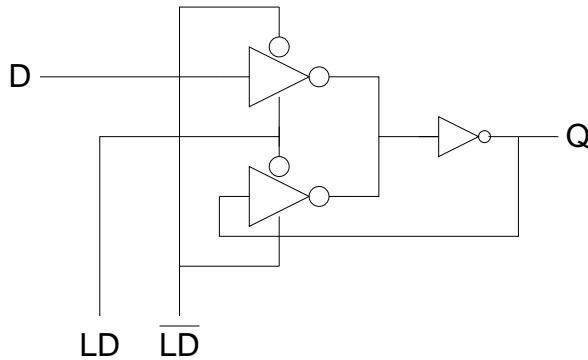
# Latches and Flip-Flops

---

- A simpler layout may be achieved using tristate inverters.




- this design requires two additional transistors but may well be more compact.
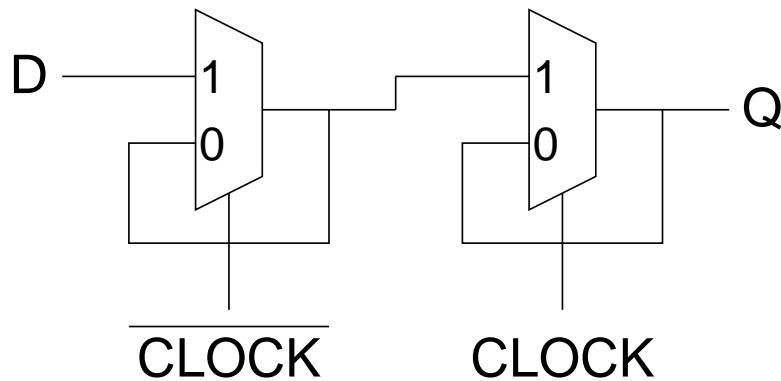
# Latches and Flip-Flops

---

- For use in simple synchronous circuits we use a pair of latches in a master slave configuration.




- this avoids the race condition in which a transparent latch drives a second transparent latch operating on the same clock phase.
- the circuit behaves as a rising edge triggered D type flip-flop.


# Latches and Flip-Flops

---

- Transmission gate implementation

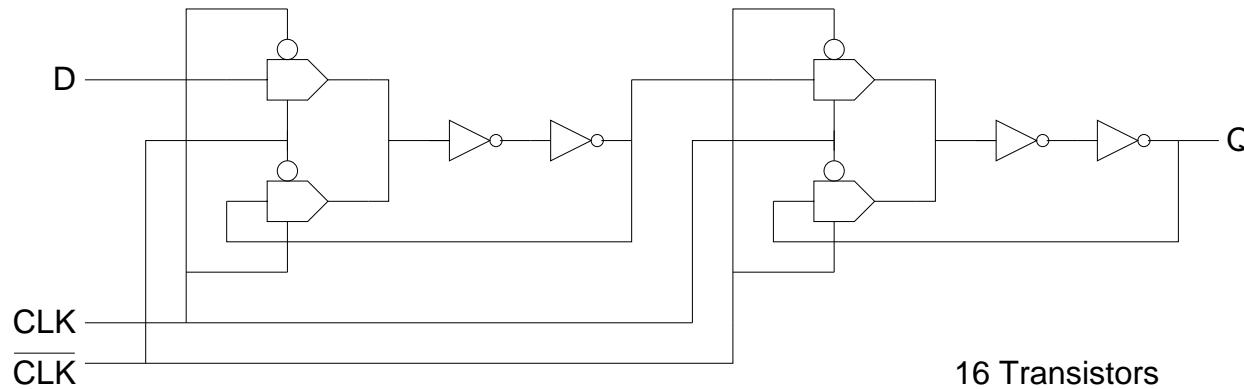


- Tristate inverter implementation

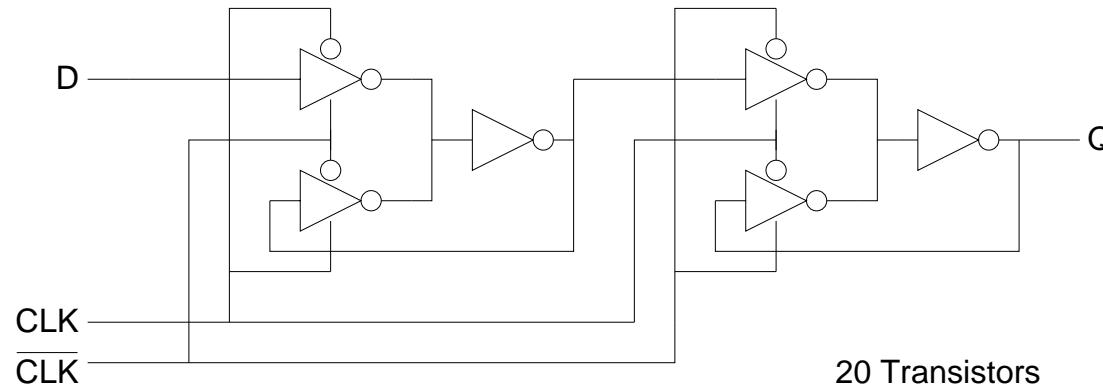


# Latches and Flip-Flops

---

- Alternative configuration

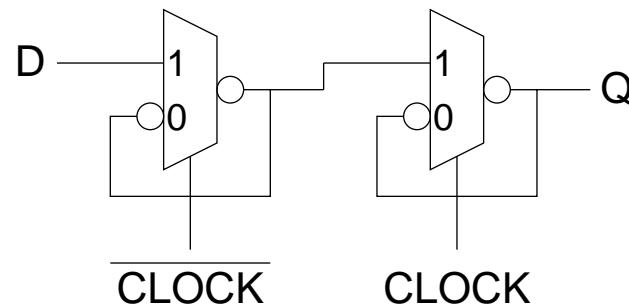



- Implementation

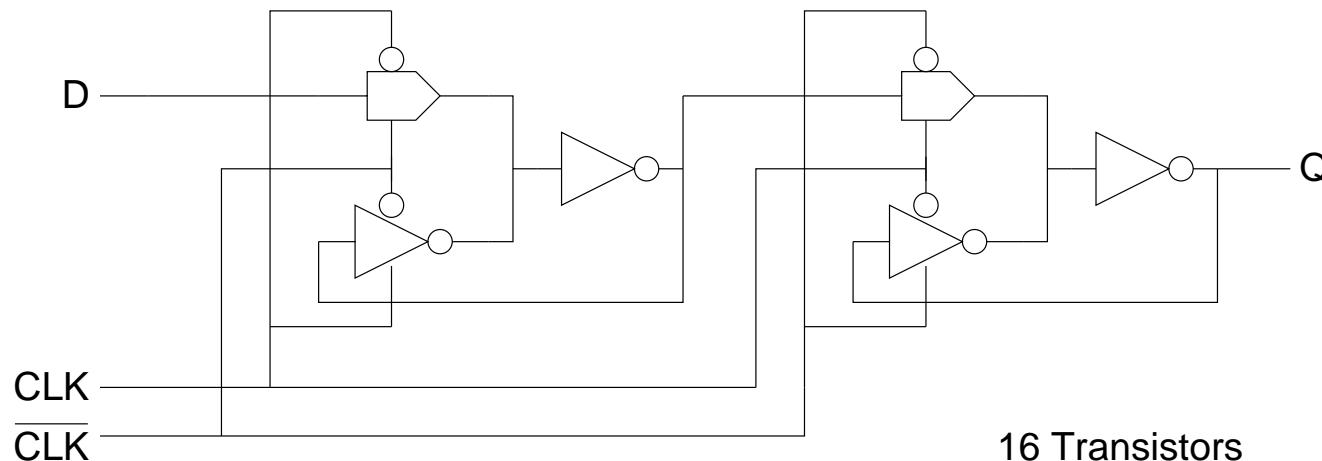

# Latches and Flip-Flops

---

- Layout of master slave D type.

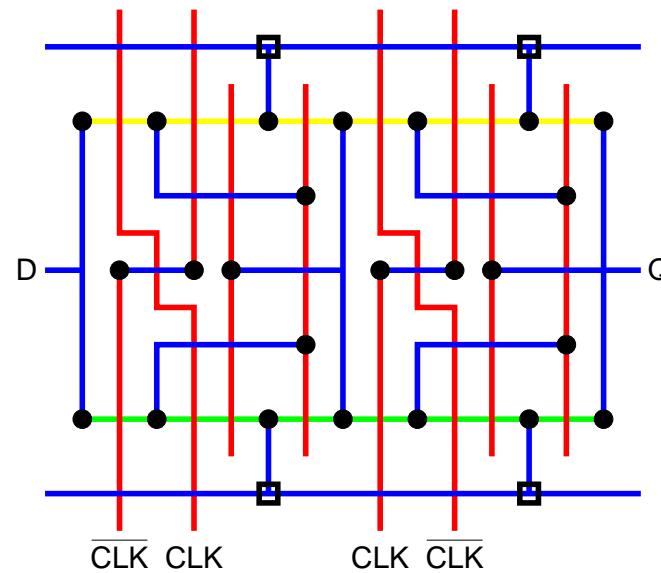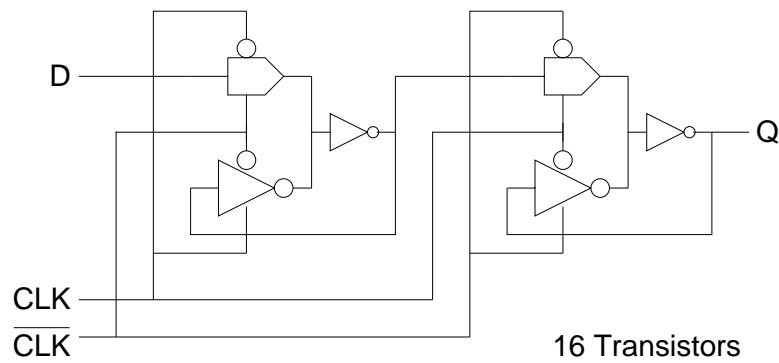


- very compact using alternative configuration.
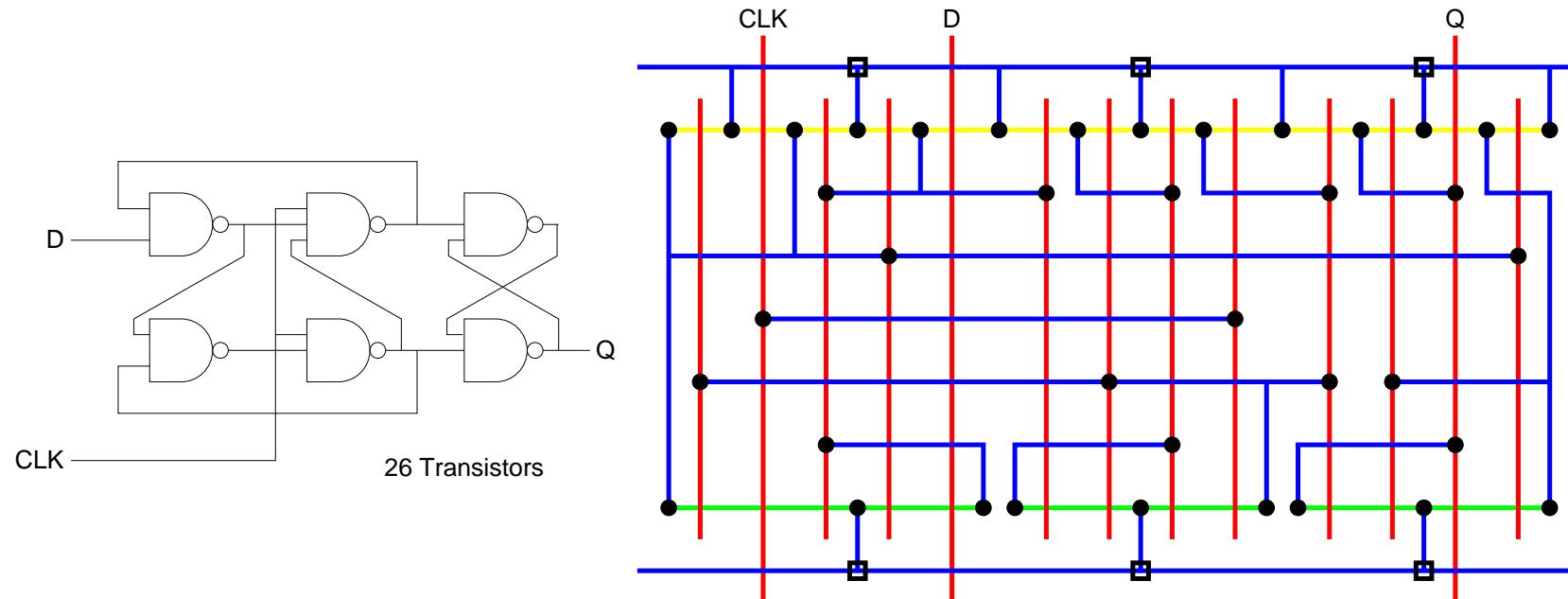
# Latches and Flip-Flops

---

- For the same functionality we could use an edge triggered D type:





- a few more transistors
- more complex wiring
- simpler clock distribution
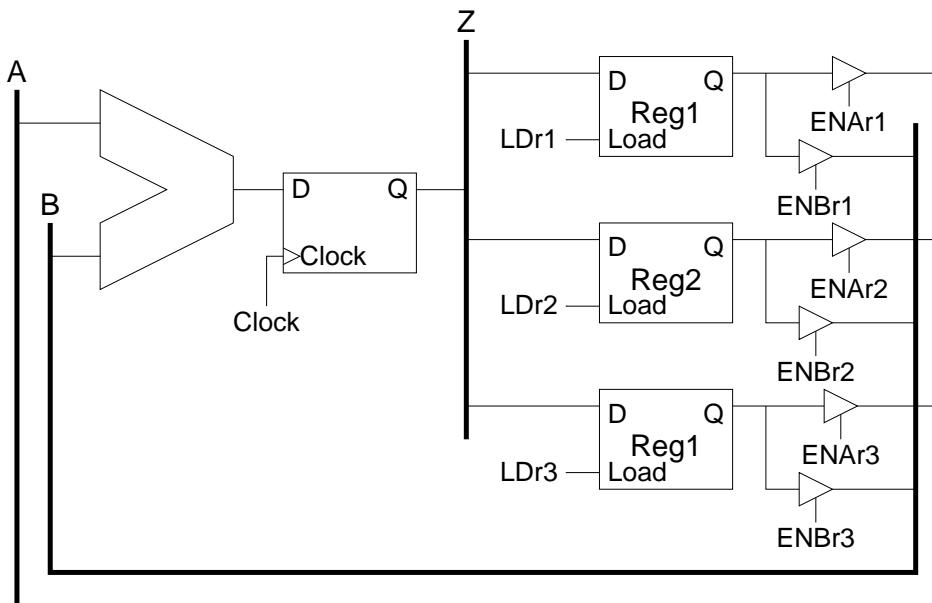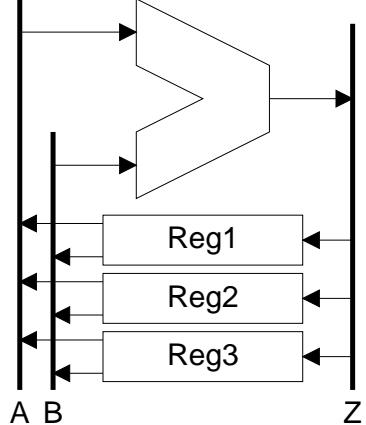
# Register File

---

Where we have large amounts of storage the use of individual latches can lead to space saving.



- Load signals must be glitch free with tightly controlled timing.
- Edge Triggered D-type prevents a race condition ( $Reg1 \leftarrow Reg1 + Reg2$ ).