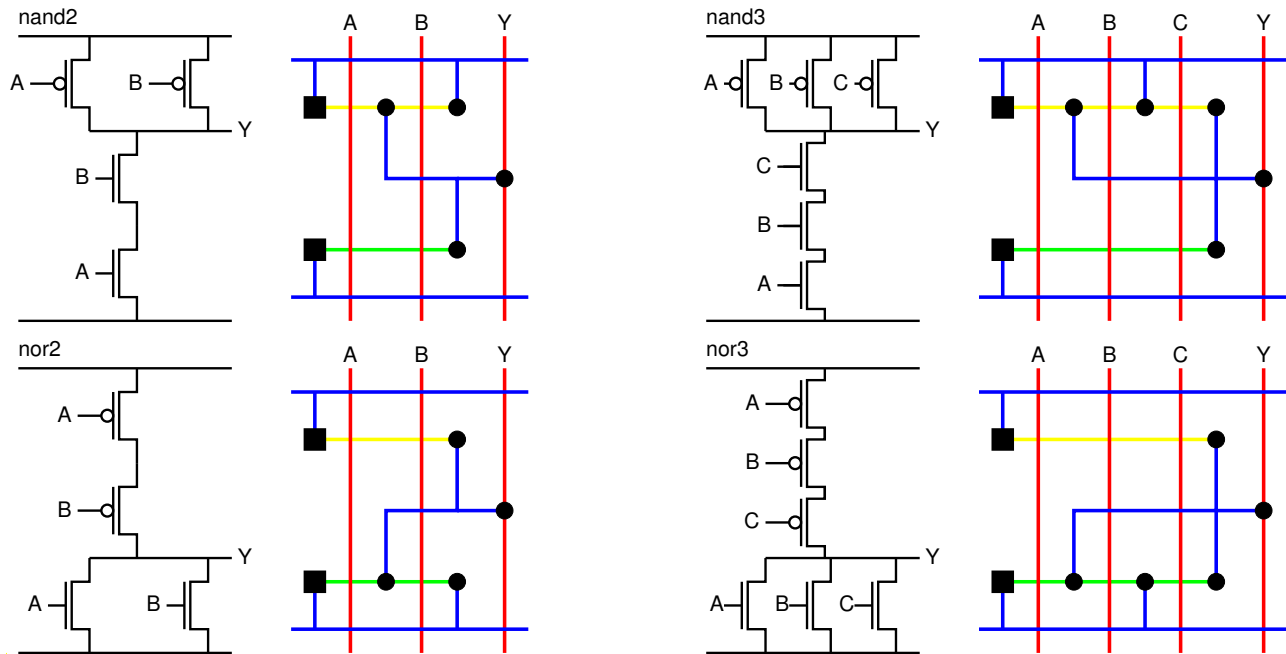


Mini Design Exercise 1

Design a 2 or 3 input NAND or NOR gate using AMS 0.35 μm technology (c35b4) based on the appropriate stick diagram shown here¹.




Optimize the gate for equal average rise and fall times based on restrictions you are given².

¹start by editing your inverter and saving with a new name rather than starting from scratch

²type `get_desex1_restriction` at the unix command prompt to find your personal restrictions

Mini Design Exercise 1

Measurements

 


- Propagation delays are measured based on 50% of V_{DD} .
- Rise and fall times are based on 10% and 90% of V_{DD} .

Mini Design Exercise 1

Simulation Conditions

The measured performance of a gate will depend on the input drive conditions and the output load conditions. For useful results we must ensure realistic drive and load conditions.

 - Don't allow two inputs to change simultaneously.




Mini Design Exercise 1

Simulation Conditions

- All simulations loaded³

 Load should be in proportion to the load experienced in a real circuit.




Where a NAND gate is used as the load, tie unused inputs to V_{DD} . Where a NOR gate is used as the load, tie unused inputs to GND.

³remember to record the results at Y rather than at the output of one of the load devices!

Mini Design Exercise 1

Simulation Conditions

 - reasonable input slopes
 - not much faster nor much slower than the resulting output slope




Mini Design Exercise 1

Advanced Simulation

HSpice's sweep facility allows you to run several different simulations in one batch and then select the simulation which gives the best results for further development. See the following web page for more information:
 
<https://secure.ecs.soton.ac.uk/notes/bim/notes/vlsi/assign/sweep.html>



Remember to update the Magic files and recreate the HSpice netlist before final submission.

Mini Design Exercise 1

Deliverables

- Files

The following files must exist in your home file store before the submission process begins⁴:

- `~/design/magic/desex1/<cellname>.mag`
- `~/design/magic/desex1/<cellname>_ld.mag`
- `~/design/magic/desex1/<cellname>_ld.sp`
- `~/design/magic/desex1/<cellname>_ld.spice`

- Information

- Transistor size information: W_N, W_P (in microns, μm)
- Rise and Fall information: t_r, t_f (in picoseconds, ps)

- Documentation

No documentation is required for this exercise other than an up to date log book.

⁴where `<cellname>` is `nand2`, `nand3`, `nor2` or `nor3`

Mini Design Exercise 1

Handin & Deadline

- Preparation For Handin

Run the following script to collect together the files for handin. (This script will also prompt you for the information that you have collected.)

```
prepare_vlsi desex1
```

The script will create a single file

```
~/design/magic/desex1/handin.tar
```

for the next stage of handin.

- Electronic Handin

The Computer-Based Assignment Submissions System at

```
https://handin.ecs.soton.ac.uk/
```

will guide you through the stages required to upload the `handin.tar` file.

- The Deadline for this exercise is *16:00 on Wednesday 23rd October.*